

R16

Code No: 133AJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, April/May - 2018

DIGITAL LOGIC DESIGN

(Common to CSE, IT)

Max. Marks: 75

Time: 3 Hours

Note: This question paper contains two parts A and B.  
Part A is compulsory which carries 25 marks. Answer all questions in Part A.  
Part B consists of 5 Units. Answer any one full question from each unit.  
Each question carries 10 marks and may have a, b, c as sub questions.

PART- A

(25 Marks)

- 1.a) Convert  $(67A9)_{16}$  into decimal. [2]
- b) Add (+80) and (-70) using 2's complement. [3]
- c) Write the truth table of Ex-OR Gate. [2]
- d) Implement OR gate using NAND gates only. [3]
- e) Write the truth table of half adder. [2]
- f) Design half subtractor circuit. [3]
- g) Differentiate between Latch and flip flop. [2]
- h) Draw the circuit diagram of Ring counter. [3]
- i) Differentiate between RAM and ROM. [2]
- j) Name any 3 logic micro operations. [3]

PART-B

(50 Marks)

- 2.a) i) Convert  $(657)_8$  into decimal.  
ii) Convert  $(2348)_{10}$  into hexa decimal.
- b) Represent the decimal number 46.5 as a floating point number with 16 bit mantissa and 8 bit exponent. [5+5]

OR

- 3.a) i) Convert 110001.1010010 into hexadecimal.  
ii) Convert  $(423.25)_{10}$  into Hex.
- b) i) Simplify  $A(B+C)+AB+ABC$   
ii) Write the truth table and symbols of AND and OR gates. [5+5]

4. Obtain the simplified expression in sum of products for the following Boolean function.  
a)  $F(A,B,C,D) = \sum(2,3,12,13,14,15)$ . [5+5]  
b)  $BDE+B'CD+CDE+ABCE+ABC'DE'$

OR

5. Obtain the simplified expression in product of sums.  
a)  $F(A,B,C,D) = \pi(0,1,2,3,4,10,11)$  [5+5]  
b)  $F(A,B,C,D) = \pi(1,3,5,7,13,15)$

- 6.a) Design half adder using only NAND gates. [5+5]  
b) Design a combinational circuit which converts BCD to Excess-3 code.

OR

- 7.a) Design a 2 bit magnitude comparator. [5+5]  
b) Implement  $4 \times 16$  decoder using two  $3 \times 8$  decoders.

- 8.a) Explain a right shift register. [5+5]  
b) Design a 3 bit Ripple counter.

OR

- 9.a) What is a hazard? How do you eliminate hazards? [5+5]  
b) Design and explain Johnson counter.

- 10.a) Explain different types ROMs.  
b) Implement the following Boolean functions using PLA with 3 AND gates. [5+5]  
 $F_1(ABC) = \sum(3,5,7)$ ,  $F_2 = \sum(4,5,7)$ .

OR

- 11.a) Explain the applications of Logic micro operations. [5+5]  
b) Explain shift Right and Left with examples.

---0000---