

R15

Code No: 124DH

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, April - 2018

PRINCIPLES OF ELECTRICAL ENGINEERING

(Common to ECE, ETM)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.
Part A is compulsory which carries 25 marks. Answer all questions in Part A.
Part B consists of 5 Units. Answer any one full question from each unit.
Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(25 Marks)

- 1.a) What is transient response of circuit? [2]
- b) What are initial conditions? Explain their significance. [3]
- c) What are symmetrical networks? [2]
- d) Define Z parameters. Give the symmetry and reciprocity conditions in terms of z-parameters. [3]
- e) What is characteristic impedance? [2]
- f) What are different types of filters? [3]
- g) What is the basic principle of DC generator? [2]
- h) List out the different types of DC motor. [3]
- i) State the applications of stepper motor. [2]
- j) Draw the No-load vector diagram of 1- ϕ transformer. [3]

PART-B

(50 Marks)

- 2.a) Determine the current i for $t \geq 0$ if initial current $i(0) = 1$ for the circuit shown in Figure 1.

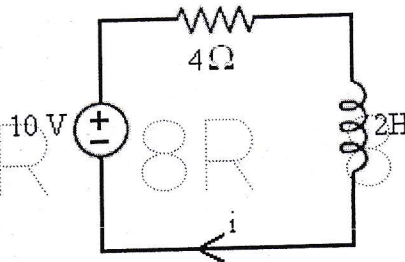


Figure: 1

- b) Switch is opened at $t = 0$ in the circuit shown in Figure 2. Then find the current ' i '. [5+5]

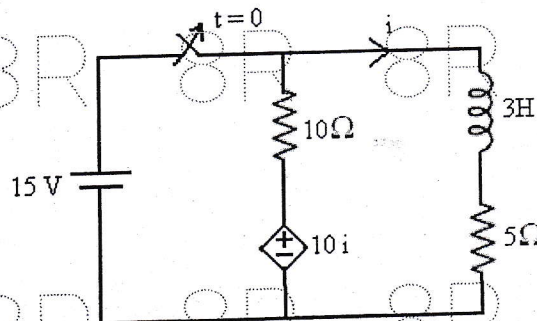


Figure: 2

OR

- 3.a) Obtain the transient response for source free series R-L circuit.
b) Obtain the transient response for source free series R-C circuit.

[5+5]

4. Find Z and Y parameter of the network shown below Figure. 3.

[10]

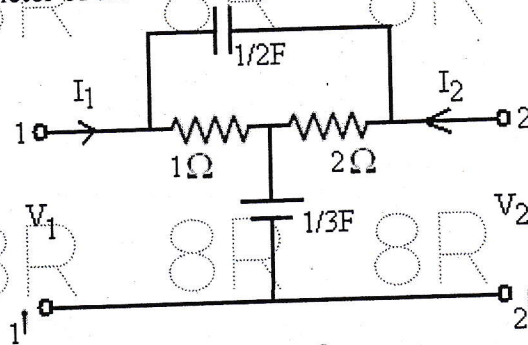


Figure: 3

OR

- 5.a) Derive the relationship between Z parameters and Y parameters.
b) Find ABCD parameters of the following network shown in figure 4.

[5+5]

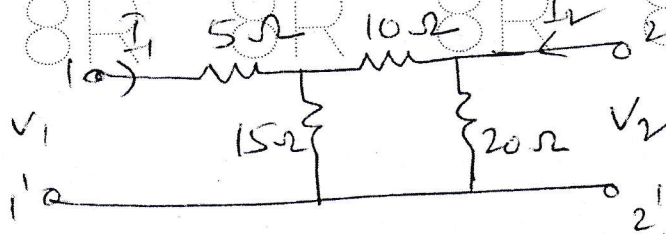


Figure: 4

6. Explain π - type attenuator and also design it to give 20db attenuation and to have characteristic impedance of 100Ω .

[10]

OR

- 7.a) Draw a circuit of a band stop filter and explain its working with neat reactance curves.
b) What are the disadvantages of proto type filters?

[6+4]

8. What are the different types of dc generators? Show the connection diagrams and load characteristics of each type.

[10]

OR

- 9.a) Explain the principle operation of dc motor.
b) Explain the Swinburne's test to be conducted on d.c machine.

[5+5]

- 10.a) Explain the principle operation of transformer.
b) Explain the losses in a transformer.

[5+5]

OR

11. A 50Hz, 1 ϕ , 100 KVA transformer has full load copper loss of 1200W and its iron loss is 960W. Calculate:

- a) The efficiency at full load, unity power factor.
b) The efficiency at half load, 0.8 power factor.
c) The efficiency at 7.5% of full load, 0.7 power factor.

[10]