

Code No: 5177F

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

M.Tech I Semester Examinations, February - 2014

DIGITAL SYSTEM DESIGN

(Embedded Systems and VLSI Design)

Time: 3 Hours

Max. Marks: 60

**Instructions:**

- i) Part A is compulsory Question for 20 marks.
- ii) Part B consists of five questions with "either" "or" pattern. The student has to answer any one. However students have to answer five questions from Part B (numbered from 2 to 6)

**PART - A**  
(Answer all sub questions)

5 × 4 marks = 20

- 1.a) Discuss in detail about reduction of state tables and state assignments.
- b) Discuss in detail about bridging faults.
- c) Draw the circuit which realizes the function  $f(x) = x_1 x_2 + x_3 x_4$  using AND-OR gates using Boolean difference method. Obtain the test set to detect SAO fault on input line  $x_1$  of this circuit.
- d) Discuss the algorithmic steps involved in PODEM.
- e) Discuss about the circuit test approach.

**PART - B**


5 × 8 marks = 40

Answer either "a" or "b" from each question, but not both

- 2.a) Draw an ASM chart for the control logic of a binary multiplier. Realize the same using MUX, decoder and D-type flip flops.

**OR**

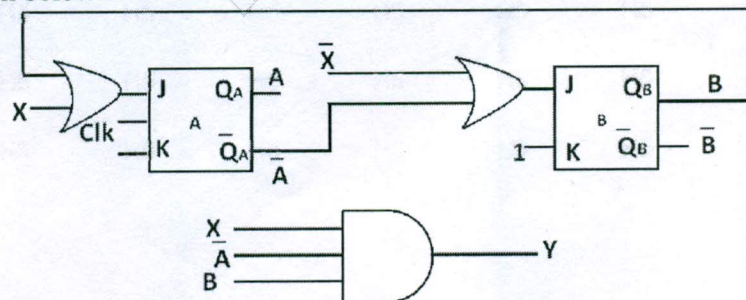- b) Derive the state equation, state table and state diagram for the sequential circuit shown below




- 3.a) i) Explain about various timing issues in any digital system with neat diagrams.  
ii) Highlight the differences between ROM, PLA and PAL.

**OR**

- b) i) Discuss design of:
  - (1) Array multiplier
  - (2) Shift and add multiplier.
- ii) List out the merits and demerits of the above two approaches.




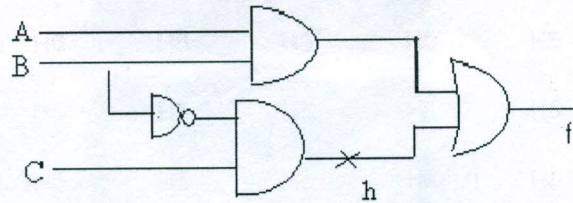- 4.a) Apply D-algorithm to detect SAO fault at 'h' in the given circuit and establish the test vectors.



OR

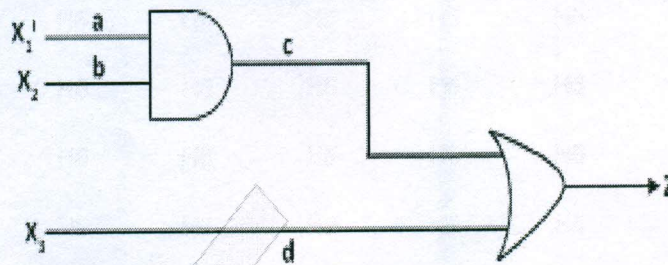- b) Draw the table giving the set of possible single stuck at faults and fault free responses and also construct the fault cover table for the circuit shown below.



- 5.a) Explain how Kohavi algorithm can be used for detection of faults. Describe based on an example.

OR

- b) Describe how signature analysis is done. Highlight its suitability for detecting bridging faults.
- 6.a) Discuss about the transition check approach.

OR

- b) Draw the ASM chart to detect the overlapping sequence 1010 from the incoming bit stream and output 1 for each detection.

Ex: x: 101010110-----  
Z: 00010101000-----

---oo0oo---