

Code No: 53025

R09

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD

B.Tech II Year I Semester Examinations, May/June - 2015

BASIC ELECTRICAL ENGINEERING

(Common to CSE, IT)


Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) What are Passive and Active elements.
b) Two coils connected in parallel across 100 V DC supply, takes 10 A current from the Supply. Power dissipated in one coil is 600 W. Find:
i) What is the resistance of that coil?
ii) What is the current flowing through that coil? [7+8]

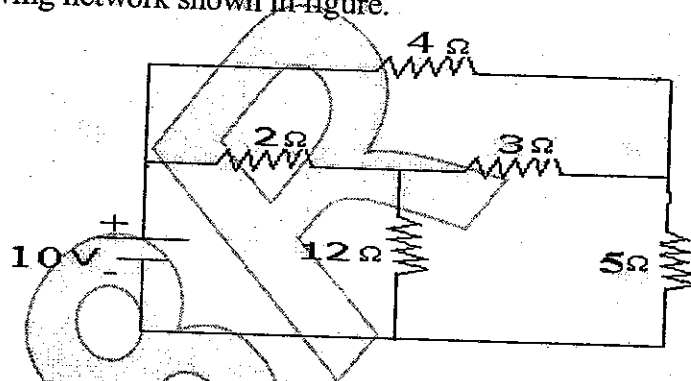- 2.a) State and explain Maximum power transfer theorem.
b) Find the current supplied by 10 V battery by using Star-Delta transformation for the following network shown in-figure. [7+8]



- 3.a) Show that power dissipated by a pure capacitor excited by a sinusoidal voltage source $V = V_m \sin(\omega t)$ is Zero.
b) An alternating current is expressed as $I = 14.14 \sin 314t$. Determine:
i) Maximum current ii) RMS current
iii) Frequency iv) Instantaneous current when $t = 0.03\text{ms}$. [7+8]
- 4.a) Explain the construction of a single phase transformer.
b) Discuss in detail the difference between a core type and a shell type transformer. [8+7]
- 5.a) Derive EMF equation of a D.C generator.
b) A 250 V dc shunt machine has line current of 80 A. It has armature and field resistances of 0.1 ohms and 125 ohms respectively. Calculate power developed in armature when running as Generator [7+8]
- 6.a) Give the classification of d.c. motors.
b) A 120 V DC shunt motor has an armature resistance of 0.2 ohms and a field resistance of 60 ohms. The full-load line current is 60A and full load speed is 1800 rpm. If the brush contact drop is 3V, find the speed of the motor at half load. [9+6]