

Code No: 53009

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year I Semester Examinations, February/March - 2016****ELECTRONIC DEVICES AND CIRCUITS****(Common to EEE, ECE, CSE, EIE, IT, MCT, ETM)****Time: 3 hours****Max. Marks: 75****Answer any five questions****All questions carry equal marks**

- 1.a) Draw the energy band diagram of a PN junction and explain the working of a Diode.
- b) Describe the piecewise linear approximation model of a diode. [9+6]
- 2.a) With a neat diagram and wave forms explain the working of a Full Wave Rectifier.
- b) Explain how Zener Diode can be used as Voltage Regulator. [8+7]
- 3.a) Explain the current components of NPN Transistor when it is operated in active region.
- b) Explain the input and output characteristics of a transistor in CB configuration. [7+8]
- 4.a) Discuss the terms Thermal Runaway and Thermal Stability?
- b) Explain how do you draw D.C and A.C load lines for amplifier circuit? [6+9]
- 5.a) Justify the validity of approximate hybrid model of a transistor applicable in low frequency range.
- b) Draw the circuit diagram of CC amplifier and explain its working. [7+8]
- 6 a) With the help of neat sketches and characteristic curves explain the operation of the junction FET.
- b) Explain the construction of MOSFET. [7+8]
- 7.a) Draw the circuit diagram of CS amplifier and explain its working.
- b) Compare FET with BJT. [9+6]
- 8.a) Draw the two transistor model of an SCR and explain its breakdown operation.
- b) Explain the principle behind the Varactor diode and list out its application. [8+7]

---ooOoo---