

R13

Code No: 115EB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, March - 2017

LINEAR AND DIGITAL IC APPLICATIONS

(Common to BME, ECE, ETM)

Time: 3 hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A

(25 Marks)

- 1.a) Show the standard representation of IC voltage regulator. [2]
- b) Explain the precautions that can be taken to minimize the effect of noise on an OP-AMP circuit. [3]
- c) Define stable and quasi stable state. [2]
- d) Draw the circuit diagram of Second order high pass filter and give its transfer function. [3]
- e) List out different types of A/D converters. [2]
- f) What do you mean by quantization error in an A/D converter? [3]
- g) Give the working principle of analog multiplexer. [2]
- h) How to interface the TTL logic gates to the CMOS logic? [3]
- i) What is meant by state diagram? [2]
- j) Write the specifications of counter IC's. [3]

PART - B

(50 Marks)

2. Design a differentiator circuit that will differentiate input signal with $f_{\max} = 100\text{Hz}$. [10]

OR

- 3.a) What are the differences between the inverting and non inverting terminals? What do you mean by the term "virtual ground"? [5+5]
- b) Explain the method of boosting the current of a three terminal voltage regulator. [5+5]

4. Design and explain the operation of All Pass Filter with its characteristics. [10]

OR

- 5.a) Draw the circuit of Schmitt trigger using 555 timer and explain its operation. [5+5]
- b) Draw the circuit of a PLL AM detector and explain its operation. [5+5]

6. Draw the schematic block diagram of Dual-slope A/D converter and explain its operation. Derive expression for its output voltage V_o . [10]

OR

- 7.a) What is the conversion time of a 10 bit successive approximation ADC if its input clock is 5 MHz? [5+5]
- b) List the specifications of DAC. [5+5]

8.a) Design a 5 to 32 line decoder using 3 to 8 line decoder, active low outputs with 2 active low and one active high enable.

b) What do you mean by Carry propagation delay? Design a 4-bit Carry look ahead generation circuit? [5+5]

OR

9. Draw and explain the block diagram of n-bit parallel binary adder/subtractor. [10]

10.a) Explain operation of DRAM cell array.

b) Design and implement FIFO shift register using IC's. [5+5]

OR

11.a) Design and implement 4-bit synchronous down counter using IC.

b) Explain the internal structure of ROM. [5+5]

---ooOoo---