

## II B.Tech II Semester Examinations, April/May 2012

**PULSE AND DIGITAL CIRCUITS**

Common to BME, ICE, E.COMP.E, ETM, E.CONT.E, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

- Explain the response of the clamping circuit when a square wave input is applied under steady state conditions.
  - Explain the effect of diode characteristics on clamping voltage. [8+8]
- Draw the circuit diagram of UJT sweep circuit and explain its operation with necessary waveforms.
  - Derive the expression for sweep speed error of a transistor constant current sweep circuit. [16]
- Discuss the applications of RC integrator and differentiator in brief.
  - Explain the operation of RC low pass circuit for exponential input. [8+8]
- Explain about various switching conditions of Schmitt trigger with necessary waveforms. [16]
- Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
  - For the figure 5b given below, draw the output waveform X for the given inputs.

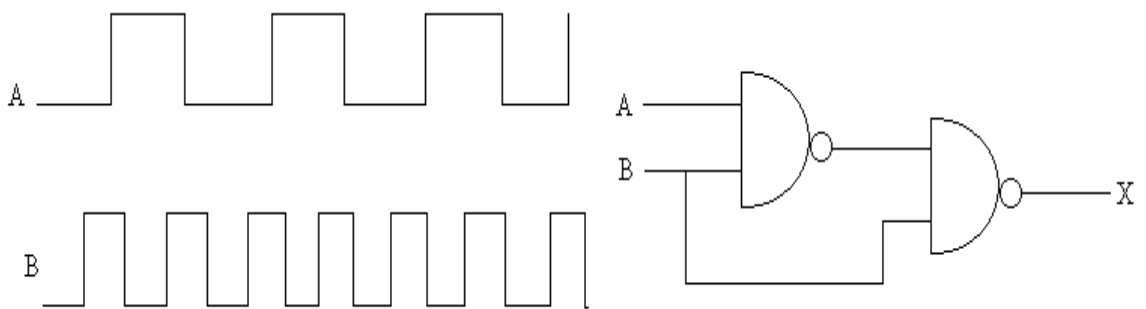


Figure 5b

[8+8]

- Define phase delay and phase jitter?
  - Explain the method of synchronization of a sinusoidal oscillator with pulses.
  - Explain the frequency division in sweep circuit. [4+8+4]
- For a common emitter circuit  $V_{cc} = 10V$ ,  $R_c = 1k\Omega$ ,  $I_B = 0.2A$ . Determine
    - The value of  $h_{FE}(\text{min})$  for saturation to occur.
    - If  $R_c$  is changed to  $220\Omega$ , will the transistor be saturated?

Code No: 07A4EC07

**R07**

**Set No. 2**

- (b) Explain the phenomenon of latching in a transistor. [8+8]
8. (a) Draw the bidirectional gate using transistors and explain its working.
- (b) Discuss the reduction of pedestal in a sampling gate circuit. [16]

\*\*\*\*\*

## II B.Tech II Semester Examinations, April/May 2012

## PULSE AND DIGITAL CIRCUITS

Common to BME, ICE, E.COMP.E, ETM, E.CONT.E, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

- Draw the circuit diagram of UJT sweep circuit and explain its operation with necessary waveforms.
  - Derive the expression for sweep speed error of a transistor constant current sweep circuit. [16]
- Draw the bidirectional gate using transistors and explain its working.
  - Discuss the reduction of pedestal in a sampling gate circuit. [16]
- For a common emitter circuit  $V_{cc} = 10V$ ,  $R_c = 1k\Omega$ ,  $I_B = 0.2A$ . Determine
    - The value of  $h_{FE}(\min)$  for saturation to occur.
    - If  $R_c$  is changed to  $220\Omega$ , will the transistor be saturated?
  - Explain the phenomenon of latching in a transistor. [8+8]
- Explain about various switching conditions of Schmitt trigger with necessary waveforms. [16]
- Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
  - For the figure 5b given below, draw the output waveform X for the given inputs.

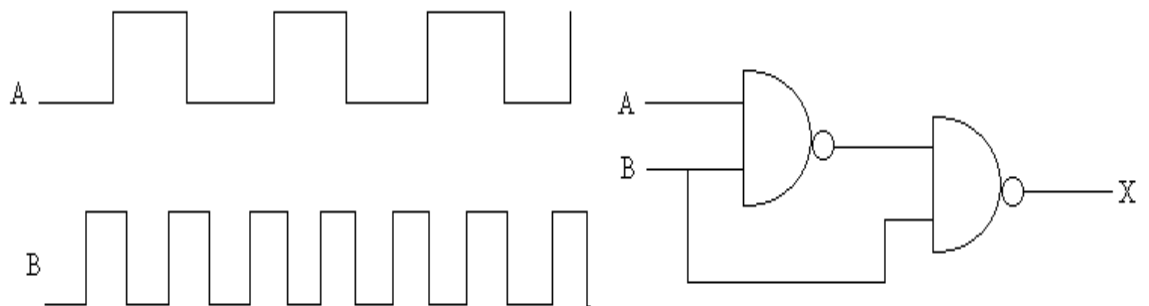


Figure 5b

[8+8]

- Explain the response of the clamping circuit when a square wave input is applied under steady state conditions.
  - Explain the effect of diode characteristics on clamping voltage. [8+8]
- Discuss the applications of RC integrator and differentiator in brief.
  - Explain the operation of RC low pass circuit for exponential input. [8+8]

Code No: 07A4EC07

**R07**

**Set No. 4**

8. (a) Define phase delay and phase jitter?  
(b) Explain the method of synchronization of a sinusoidal oscillator with pulses.  
(c) Explain the frequency division in sweep circuit. [4+8+4]

\*\*\*\*\*

## II B.Tech II Semester Examinations, April/May 2012

## PULSE AND DIGITAL CIRCUITS

Common to BME, ICE, E.COMP.E, ETM, E.CONT.E, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

- Discuss the applications of RC integrator and differentiator in brief.
  - Explain the operation of RC low pass circuit for exponential input. [8+8]
- Explain the response of the clamping circuit when a square wave input is applied under steady state conditions.
  - Explain the effect of diode characteristics on clamping voltage. [8+8]
- Draw the bidirectional gate using transistors and explain its working.
  - Discuss the reduction of pedestal in a sampling gate circuit. [16]
- Draw the circuit diagram of UJT sweep circuit and explain its operation with necessary waveforms.
  - Derive the expression for sweep speed error of a transistor constant current sweep circuit. [16]
- Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
  - For the figure 5b given below, draw the output waveform X for the given inputs.

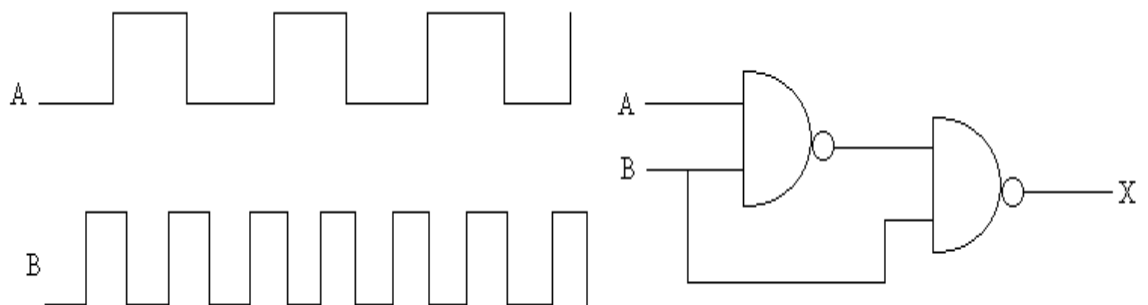


Figure 5b

[8+8]

- Explain about various switching conditions of Schmitt trigger with necessary waveforms. [16]
- For a common emitter circuit  $V_{cc} = 10V$ ,  $R_c = 1k\Omega$ ,  $I_B = 0.2A$ . Determine
    - The value of  $h_{FE}(\min)$  for saturation to occur.
    - If  $R_c$  is changed to  $220\Omega$ , will the transistor be saturated?
  - Explain the phenomenon of latching in a transistor. [8+8]

Code No: 07A4EC07

**R07**

**Set No. 1**

8. (a) Define phase delay and phase jitter?  
(b) Explain the method of synchronization of a sinusoidal oscillator with pulses.  
(c) Explain the frequency division in sweep circuit. [4+8+4]

\*\*\*\*\*

## II B.Tech II Semester Examinations, April/May 2012

## PULSE AND DIGITAL CIRCUITS

Common to BME, ICE, E.COMP.E, ETM, E.CONT.E, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Discuss the applications of RC integrator and differentiator in brief.  
(b) Explain the operation of RC low pass circuit for exponential input. [8+8]
2. (a) Draw the bidirectional gate using transistors and explain its working.  
(b) Discuss the reduction of pedestal in a sampling gate circuit. [16]
3. (a) Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.  
(b) For the figure 3b given below, draw the output waveform X for the given inputs.

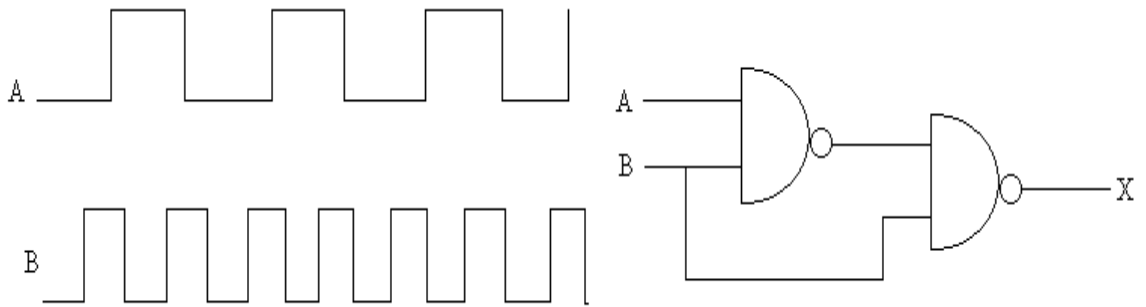


Figure 3b

[8+8]

4. (a) Explain the response of the clamping circuit when a square wave input is applied under steady state conditions.  
(b) Explain the effect of diode characteristics on clamping voltage. [8+8]
5. (a) Define phase delay and phase jitter?  
(b) Explain the method of synchronization of a sinusoidal oscillator with pulses.  
(c) Explain the frequency division in sweep circuit. [4+8+4]
6. (a) Draw the circuit diagram of UJT sweep circuit and explain its operation with necessary waveforms.  
(b) Derive the expression for sweep speed error of a transistor constant current sweep circuit. [16]
7. (a) For a common emitter circuit  $V_{cc} = 10V$ ,  $R_c = 1k\Omega$ ,  $I_B = 0.2A$ . Determine
  - i. The value of  $h_{FE}(\min)$  for saturation to occur.

Code No: 07A4EC07

**R07**

**Set No. 3**

- ii. If  $R_c$  is changed to  $220\Omega$ , will the transistor be saturated?
- (b) Explain the phenomenon of latching in a transistor. [8+8]
8. Explain about various switching conditions of Schmitt trigger with necessary waveforms. [16]

\*\*\*\*\*