

II B.Tech II Semester Examinations, April/May 2012**SWITCHING THEORY AND LOGIC DESIGN****Common to Electronics And Telematics, Electronics And Communication Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions
All Questions carry equal marks**

1. Draw an ASM chart for the state table given below. Design a control unit with the help of D-Flip flop and decoders. [16]

PS	NS	
	X = 0	X = 1
000	011,0	100,1
001	001,0	100,1
010	010,0	000,1
011	001,0	010,1
100	010,0	011,0

2. (a) Draw the block diagram of a ROM. Define address and word. Relate the number of output lines with number of bits in a word. How an output word can be selected?
(b) For a 64×8 ROM, determine the number of words it contains and the size of each word. How many output lines are there for the ROM? [8+8]
3. (a) Give a brief description about the following number systems with suitable examples.
- Decimal number system
 - Binary number system
 - Octal number system
 - Hexadecimal system
- (b) i. Convert $(2598.675)_{10}$ to hexadecimal
ii. Convert $(10010.1011)_2$ to decimal
iii. Convert $(10111101.01101001)_2$ to octal
iv. Convert $(465.0647)_8$ to Binary. [8+8]

4. Implement the following functions using appropriate DECODER

$$F1 = \Sigma m(2,4,6,8,12)$$

$$F2 = \Sigma m(1,3,6,7,9,10)$$

$$F3 = \Sigma m(1,3,4,5,6,9,12,14)$$

$$F4 = \Sigma m(2,4,8)$$

[16]

5. Determine the logic function produced by A and B when applied to A water pump is required to turn ON automatically whenever the water level in any two or more of three tanks A, B and C falls below a pre-set level. Each water tank is provided

with a level detector that generates a HIGH voltage whenever the water level in that tank is LOW. Derive a Switching function with minimum number of literals to implement the above situation. [16]

6. (a) Differentiate edge triggering, Level triggering and Pulse triggering.
 (b) Design a clocked JK flip flop. Explain its operation with the help of characteristic table and characteristic equation. Give the symbol of edge triggered JK flipflop. [8+8]
7. (a) Express the Boolean function:
 $F(x,y,z) = xy + x'z$ in a product of maxterm form
 (b) How many rows will be there in the truth table of a logic system having n input binary variable?
 (c) Prepare the truth table for the Boolean function
 $F(X, Y, Z) = X(YZ' + Y'Z)$ [8+2+6]
8. Determine a minimal state table equivalent to the state table given below. [16]

PS	NS,Z	
	J1	J2
I1	I4,0	I2,1
I2	I7,0	I1,0
I3	I4,0	I2,1
I4	I3,0	I2,1
I5	I4,0	I1,1
I6	I5,1	I6,1
I7	I5,1	I6,1

II B.Tech II Semester Examinations, April/May 2012**SWITCHING THEORY AND LOGIC DESIGN****Common to Electronics And Telematics, Electronics And Communication Engineering****Time: 3 hours****Max Marks: 80**

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Give a brief description about the following number systems with suitable examples.
 - i. Decimal number system
 - ii. Binary number system
 - iii. Octal number system
 - iv. Hexadecimal system
- (b)
 - i. Convert $(2598.675)_{10}$ to hexadecimal
 - ii. Convert $(10010.1011)_2$ to decimal
 - iii. Convert $(10111101.01101001)_2$ to octal
 - iv. Convert $(465.0647)_8$ to Binary. [8+8]
2. Implement the following functions using appropriate DECODER

$F1 = \Sigma m(2,4,6,8,12)$
 $F2 = \Sigma m(1,3,6,7,9,10)$
 $F3 = \Sigma m(1,3,4,5,6,9,12,14)$
 $F4 = \Sigma m(2,4,8)$ [16]
3. (a) Draw the block diagram of a ROM. Define address and word. Relate the number of output lines with number of bits in a word. How an output word can be selected?

(b) For a 64×8 ROM, determine the number of words it contains and the size of each word. How many output lines are there for the ROM? [8+8]
4. (a) Differentiate edge triggering, Level triggering and Pulse triggering.

(b) Design a clocked JK flip flop. Explain its operation with the help of characteristic table and characteristic equation. Give the symbol of edge triggered JK flipflop. [8+8]
5. Draw an ASM chart for the state table given below. Design a control unit with the help of D-Flip flop and decoders. [16]

PS	NS	
	X = 0	X = 1
000	011,0	100,1
001	001,0	100,1
010	010,0	000,1
011	001,0	010,1
100	010,0	011,0

6. Determine the logic function produced by A and B when applied to A water pump is required to turn ON automatically whenever the water level in any two or more of three tanks A, B and C falls below a pre-set level. Each water tank is provided with a level detector that generates a HIGH voltage whenever the water level in that tank is LOW. Derive a Switching function with minimum number of literals to implement the above situation. [16]
7. Determine a minimal state table equivalent to the state table given below. [16]

PS	NS,Z	
	J1	J2
I1	I4,0	I2,1
I2	I7,0	I1,0
I3	I4,0	I2,1
I4	I3,0	I2,1
I5	I4,0	I1,1
I6	I5,1	I6,1
I7	I5,1	I6,1

8. (a) Express the Boolean function:
 $F(x,y,z) = xy + x'z$ in a product of maxterm form
- (b) How many rows will be there in the truth table of a logic system having n input binary variable?
- (c) Prepare the truth table for the Boolean function
 $F(X, Y, Z) = X(YZ' + Y'Z)$ [8+2+6]

II B.Tech II Semester Examinations, April/May 2012**SWITCHING THEORY AND LOGIC DESIGN****Common to Electronics And Telematics, Electronics And Communication Engineering****Time: 3 hours****Max Marks: 80**

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Draw the block diagram of a ROM. Define address and word. Relate the number of output lines with number of bits in a word. How an output word can be selected?
- (b) For a 64×8 ROM, determine the number of words it contains and the size of each word. How many output lines are there for the ROM? [8+8]
2. (a) Express the Boolean function:
 $F(x,y,z) = xy + x'z$ in a product of maxterm form
- (b) How many rows will be there in the truth table of a logic system having n input binary variable?
- (c) Prepare the truth table for the Boolean function
 $F(X, Y, Z) = X(YZ' + Y'Z)$ [8+2+6]
3. Draw an ASM chart for the state table given below. Design a control unit with the help of D-Flip flop and decoders. [16]

PS	NS	
	X = 0	X = 1
000	011,0	100,1
001	001,0	100,1
010	010,0	000,1
011	001,0	010,1
100	010,0	011,0

4. Implement the following functions using appropriate DECODER
 $F1 = \sum m(2,4,6,8,12)$
 $F2 = \sum m(1,3,6,7,9,10)$
 $F3 = \sum m(1,3,4,5,6,9,12,14)$
 $F4 = \sum m(2,4,8)$ [16]
5. Determine the logic function produced by A and B when applied to A water pump is required to turn ON automatically whenever the water level in any two or more of three tanks A, B and C falls below a pre-set level. Each water tank is provided with a level detector that generates a HIGH voltage whenever the water level in that tank is LOW. Derive a Switching function with minimum number of literals to implement the above situation. [16]
6. (a) Differentiate edge triggering, Level triggering and Pulse triggering.

- (b) Design a clocked JK flip flop. Explain its operation with the help of characteristic table and characteristic equation. Give the symbol of edge triggered JK flipflop. [8+8]

7. Determine a minimal state table equivalent to the state table given below. [16]

PS	NS,Z	
	J1	J2
I1	I4,0	I2,1
I2	I7,0	I1,0
I3	I4,0	I2,1
I4	I3,0	I2,1
I5	I4,0	I1,1
I6	I5,1	I6,1
I7	I5,1	I6,1

8. (a) Give a brief description about the following number systems with suitable examples.

- i. Decimal number system
- ii. Binary number system
- iii. Octal number system
- iv. Hexadecimal system

- (b) i. Convert $(2598.675)_{10}$ to hexadecimal
ii. Convert $(10010.1011)_2$ to decimal
iii. Convert $(10111101.01101001)_2$ to octal
iv. Convert $(465.0647)_8$ to Binary. [8+8]

II B.Tech II Semester Examinations, April/May 2012**SWITCHING THEORY AND LOGIC DESIGN****Common to Electronics And Telematics, Electronics And Communication Engineering****Time: 3 hours****Max Marks: 80**

Answer any FIVE Questions
All Questions carry equal marks

1. Implement the following functions using appropriate DECODER
 $F1 = \Sigma m(2,4,6,8,12)$
 $F2 = \Sigma m(1,3,6,7,9,10)$
 $F3 = \Sigma m(1,3,4,5,6,9,12,14)$
 $F4 = \Sigma m(2,4,8)$ [16]

2. (a) Differentiate edge triggering, Level triggering and Pulse triggering.
 (b) Design a clocked JK flip flop. Explain its operation with the help of characteristic table and characteristic equation. Give the symbol of edge triggered JK flipflop. [8+8]

3. Determine a minimal state table equivalent to the state table given below. [16]

PS	NS,Z	
	J1	J2
I1	I4,0	I2,1
I2	I7,0	I1,0
I3	I4,0	I2,1
I4	I3,0	I2,1
I5	I4,0	I1,1
I6	I5,1	I6,1
I7	I5,1	I6,1

4. (a) Draw the block diagram of a ROM. Define address and word. Relate the number of output lines with number of bits in a word. How an output word can be selected?
 (b) For a 64×8 ROM, determine the number of words it contains and the size of each word. How many output lines are there for the ROM? [8+8]

5. Determine the logic function produced by A and B when applied to A water pump is required to turn ON automatically whenever the water level in any two or more of three tanks A, B and C falls below a pre-set level. Each water tank is provided with a level detector that generates a HIGH voltage whenever the water level in that tank is LOW. Derive a Switching function with minimum number of literals to implement the above situation. [16]

6. Draw an ASM chart for the state table given below. Design a control unit with the help of D-Flip flop and decoders. [16]

PS	NS	
	X = 0	X = 1
000	011,0	100,1
001	001,0	100,1
010	010,0	000,1
011	001,0	010,1
100	010,0	011,0

7. (a) Give a brief description about the following number systems with suitable examples.
- Decimal number system
 - Binary number system
 - Octal number system
 - Hexadecimal system
- (b) i. Convert $(2598.675)_{10}$ to hexadecimal
ii. Convert $(10010.1011)_2$ to decimal
iii. Convert $(10111101.01101001)_2$ to octal
iv. Convert $(465.0647)_8$ to Binary. [8+8]
8. (a) Express the Boolean function:
 $F(x,y,z) = xy + x'z$ in a product of maxterm form
- (b) How many rows will be there in the truth table of a logic system having n input binary variable?
- (c) Prepare the truth table for the Boolean function
 $F(X, Y, Z) = X(YZ' + Y'Z)$ [8+2+6]
