

Code No: 09A30204

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD
B.Tech II Year I Semester Examinations, November/December-2013

Electric Circuits
(Common to ECE, ETM)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Explain in detail the volt-ampere relationship of R, L and C elements with neat diagrams.
- b) What is meant by independent and dependent sources? Give examples.
- c) Find the equivalent voltage source across a, b terminals of the following Figure 1. [15]

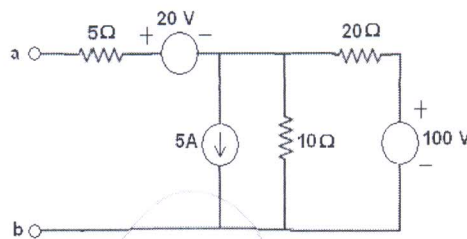


Figure: 1

- 2.a) State and explain Kirchoff's laws.
- b) Find the equivalent resistance across the terminals A-B as shown in Figure 2. [15]

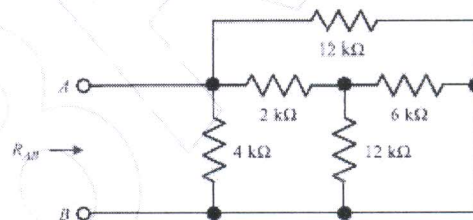


Figure: 2

- 3.a) Illustrate following terms:
 - i) Impedance
 - ii) Reactance
 - iii) Phase deference
 - iv) Power factor.
- b) A circuit consists of a resistance of 15Ω , a capacitance of $200\ \mu\text{F}$ and inductor of 0.05H all in series. If supply of 230V , 50Hz is applied to the ends of circuit. Calculate
 - i) Current in the coil
 - ii) Potential difference across each element
 - iii) Frequency at which current would have unity power factor. [15]
- 4.a) Obtain the current locus of a fixed resistance and a variable capacitance when connected with voltage of variable frequency.
- b) Given a series RLC circuit with $R = 10\ \text{ohms}$, $L = 1\ \text{mH}$ and $C = 1\ \mu\text{F}$ is connected across a sinusoidal source of $20\ \text{V}$ with variable frequency. Find
 - i) The resonant frequency
 - ii) Q factor of the circuit at resonant frequency
 - iii) Half power frequencies. [15]

8. A beam $ABCDE$, 10m long, is hinged at A and freely supported at B and D . $AB=2\text{m}$; $BD=6\text{m}$; the overhang $DE=2\text{m}$. There is a hinge at C , midway between B and D . The loading consists of a point-load of 15kN at the free end E , 20kN at the middle of BC and 40kN at the middle of CD . Evaluate the reactions at the supports. [15]

8R

- 5.a) Derive the relation between self inductance, mutual inductance and coefficient of coupling.
- b) A mild steel ring has a mean circumference of 600mm and a uniform cross-sectional area of 350 mm^2 . Calculate the MMF required producing a flux of $600 \mu\text{Wb}$ when an air gap of 1mm length is now cut in ring. Also, determine the flux produced if MMF remains constant. Given relative permeability of mild steel is 1200. [15]
6. For the network shown in Figure 3, draw the following
- Graph
 - Tree
 - Dual network. [15]

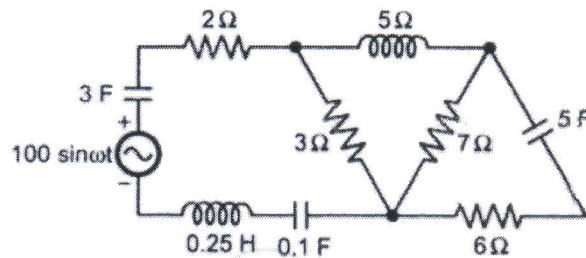


Figure: 3

- 7.a) State and explain Compensation theorem.
- b) By using Norton's theorem determine the current through 5Ω resistor (All resistances are in Ω) as shown in Figure 4. [15]

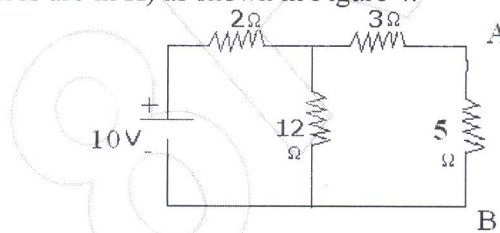


Figure: 4

- 8.a) State and explain Superposition theorem.
- b) For the network shown in Figure 5, replace the circuit to the left of terminals 'AB' with a Thevenin equivalent. The determine current in the $(2-j2) \Omega$ impedance connected to the equivalent circuit. [15]

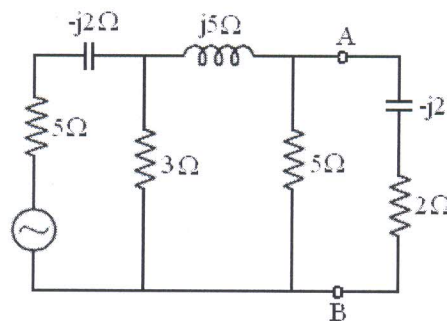


Figure: 5

---oo0oo---