

R09

Code No: 09A40403

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD**B.Tech II Year II Semester Examinations, November / December-2013****PULSE AND DIGITAL CIRCUITS****(Common to ECE, BME, ETM)****Time: 3 hours****Max. Marks: 75****Answer any five questions
All questions carry equal marks**

- 1.a) Derive an expression for the output of a high pass circuit excited by a ramp input.
b) A 1 KHz square wave output from an amplifier has rise time $t_r = 250$ ns and tilt = 10%, determine the upper and lower frequencies. [8+7]
- 2.a) Explain the response of the clamping circuit when a square wave input is applied under steady state conditions.
b) Explain the effect of diode characteristics on clamping voltage. [8+7]
- 3.a) Sketch neatly the waveforms of current & voltages for a transistor switch with capacitance loading circuit.
b) What are catching diodes? [11+4]
- 4.a) Design an astable multivibrator to generate a 5 KHz square wave with a duty cycle of 60% and amplitude 12V. Use NPN silicon transistors having $h_{FE(\min)} = 70$, $V_{CE(\text{sat})} = 0.3\text{V}$, $V_{BE(\text{sat})} = 0.7\text{V}$, $V_{BE(\text{cutoff})} = 0\text{V}$ and $R_C = 2\text{K}\Omega$.
Draw the waveforms seen at both collectors and bases.
b) Explain the operation of bistable multivibrator circuit with circuit diagram and waveform. [8+7]
- 5.a) Write the differences between the voltage and current time base generators?
b) Draw the circuit diagram and waveforms of a transistor bootstrap time base generator and explain principle of operation. [6+9]
- 6.a) Draw the circuit of an emitter-coupled bidirectional sampling gate and explain.
b) What is Pedestal? How pedestal can be reduced in a sampling gate circuit? [8+7]
- 7.a) Explain the principle of 'synchronization' and 'synchronization with frequency division'.
b) Explain the method of pulse synchronization of relaxation devices, with examples. [7+8]
- 8.a) Draw the OR gate using diodes and resistors. Verify its truth table.
b) Draw a TTL NAND gate and explain its operation. [7+8]
