

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) State and explain Kirchoff's laws.
b) By applying Kirchoff's law, find the current through all the elements in the circuit shown in figure 1.

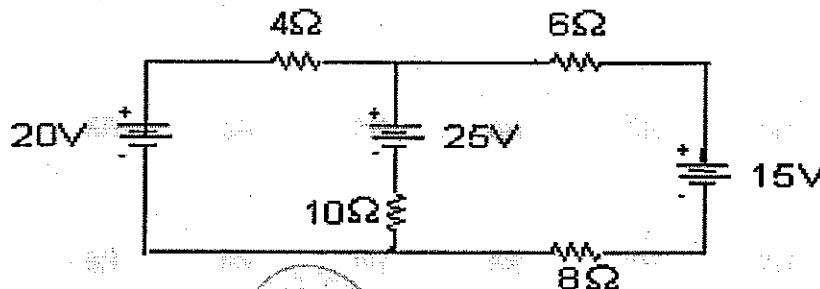


Figure: 1

- 2.a) Explain active and passive elements in detail.
b) Find the voltage across A and B terminals in the circuit shown in figure 2.

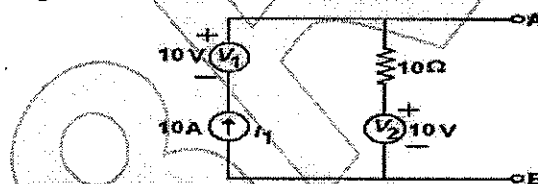


Figure: 2

3. Obtain the expression for average value, form factor and peak factor for sinusoidal wave.
4. Define efficiency and regulation of a transformer. Explain the predetermination of the efficiency and regulation with neat circuit diagrams.
- 5.a) Explain how DC generators are classified in detail.
b) A 4-pole wave connected DC generator having 60 slots on its armature with 6 conductors per slot, runs at 1000 rpm and generates an open circuit voltage of 230 V. Find the useful flux per pole.
- 6.a) Derive the torque equation of a DC motor.
b) A 4 pole, 210V wave connected shunt motor gives 10 KW when running at 750 rpm and drawing armature and field currents of 25 A and 2 A respectively. It has 320 conductors. Its resistance is 0.15. Assuming drop of 1V per brush, find:
i) total torque
ii) useful torque
iii) useful flux per pole
iv) efficiency.

- 7.a) Explain the working principle of three phase induction motor.
- b) A 6 pole induction motor is fed from 60 Hz supply. If the frequency of rotor EMF at full load is 2 Hz, find the full load speed and %slip.
- 8.a) Discuss the different types of torques required in indicating instruments.
- b) Explain the working principle of PMMC meter.

---oo0oo---

80R