

Code No: 53020

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD

B.Tech II Year I Semester Examinations, December-2014

ELECTRIC CIRCUITS

(Common to ECE, ETM)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Find the energy stored in an inductor of value 5 mH, if the current in it varies from 1 A to 5 A in 10 sec
- b) Find the value of resistor whose V-I Characteristics is given in the Figure 1 below

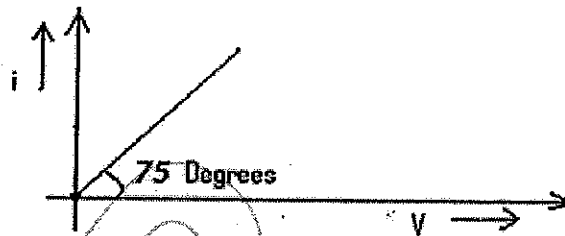


Figure 1

- c) Given the expression of charge in a capacitor $Q(V) = 3V^3 + 2V^2 + V$. Determine the value of the capacitance at $V = 2$ Volt.
 - d) A practical current source when open circuited produces 100 V and when short circuited the current in short circuit is 10 A. Find the voltage across a load of 10Ω connected to the source
 - e) Given the current passing through an element as $i(t) = 2e^{-5t}$ A. Determine the total charge passed through the element when $t = 4$ sec.
- 2.a) What does mean by super mesh and super node? Explain with examples.
 - b) For the circuit shown in Figure 2 below.

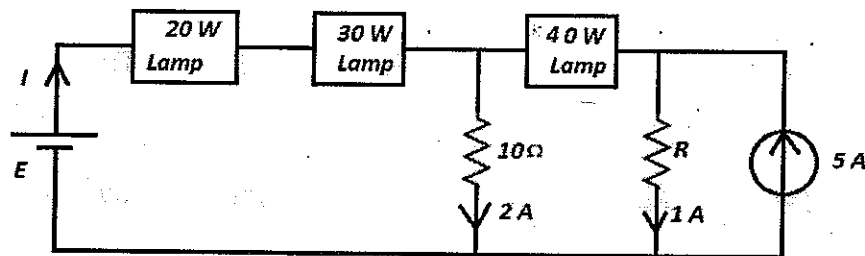


Figure 2

Find E, I, R and the voltage across 30 W Lamp.

- 6.a) Define Cutset and Tieset and find the cutset and tieset matrices by taking a suitable example
- b) Draw the graph of the following network shown in Figure 6 and from the graph find the loop currents using loop method of analysis

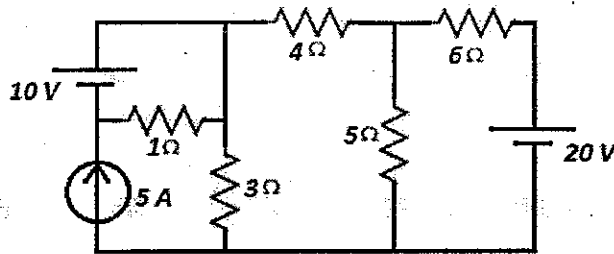


Figure 6

- 7.a) State and explain Maximum power transfer theorem with suitable example and derive the condition for maximum power transfer to the Resistive load.
- b) For the circuit diagram shown in Figure 7 below, can super position theorem be applied? Find the current in $1\ \Omega$ resistor.



Figure 7

- 8.a) For AC circuits, state and explain Millman's theorem by taking a suitable example.
- b) By taking a suitable AC circuit, explain the procedure to find Norton's current and Norton's resistance.

---oo0oo---

