

R16

Code No: 133AJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, November/December - 2017

DIGITAL LOGIC DESIGN

(Common to CSE, IT)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(25 Marks)

- 1.a) Subtract the following using 1's and 2's complement $(101)_2 - (10110)_2$. [2]
- b) Distinguish between canonical and standard forms by giving an example. [3]
- c) Derive the sum of minterms for the function $f(a,b,c)=a'b+b'c'$ [2]
- d) Implement the following function using only NAND Gates $F=a.(b'+c')+(b.c)$. [3]
- e) Differentiate multiplexer and de-multiplexer. [2]
- f) Draw the diagram of 4-Bit Parallel adder cum parallel subtractor. [3]
- g) Show the excitation table and truth table of JK flip flop. [2]
- h) Differentiate critical and non-critical race. [3]
- i) Define Register Transfer Language. [2]
- j) Differentiate PLA and PAL. [3]

PART-B

(50 Marks)

- 2.a) What are the various logic gates, give the representation along with the truth table.
 - b) What is the use of complements? Perform subtraction using 7's complement for the given Base-7 numbers $(565)-(666)$. [5+5]
- OR**
- 3.a) Convert the following to the corresponding bases
 - i) $(9BCD)_{16} = (\quad)_8$
 - ii) $(323)_4 = (\quad)_5$
 - b) Given the 8 bit data word 11011011, generate the 12 bit composite word for the Hamming code that corrects and detects single errors. [5+5]
- 4.a) Derive the product of maxterms for $f(a,b,c,d)=a.b.c+b'.d+c.d'$.
 - b) Derive and Implement Exclusive OR function involving three variables using only NAND function. [5+5]
- OR**
- 5.a) Obtain the simplified expression in SOP form of $F(a,b,c,d,e)=\sum(1,2,4,7,12,14,15,24,27,29,30,31)$ using K-maps.
 - b) Implement the function $f(a,b,c)=\pi(0,1,3,4)$ using NAND-NAND two level gate structure. [5+5]

Ro Ro Ro Ro Ro Ro Ro R

6.a) Implement an odd parity generator for 3-bit using a decoder.

b) Design a circuit for 2-bit binary multiplier.

[5+5]

Ro Ro Ro Ro **OR** Ro Ro R

7.a) Define a multiplexer? Draw a 4:1 multiplexer for the function $f(a,b,c,d) = \sum(0, 4, 5, 10, 11, 12, 15)$

b) Design a full binary adder with two half adders and an OR gate.

[5+5]

8.a) Explain about a NOR Latch in detail, with a neat diagram.

b) Design a 3-bit counter using T flip flops.

[5+5]

Ro Ro Ro Ro **OR** Ro Ro R

9. Define essential hazard? Implement SR Latch by avoiding Hazard. Neatly draw the diagram of SR latch before hazard and after Hazard elimination.

[10]

10. Explain about RAM in detail.

[10]

OR

11. What is a micro operation? List and explain its categories with relevant examples.

[10]

Ro Ro Ro Ro **---oo0oo---** Ro Ro R

Ro Ro Ro Ro Ro Ro Ro R

Ro Ro Ro Ro Ro Ro Ro R

Ro Ro Ro Ro Ro Ro Ro R

Ro Ro Ro Ro Ro Ro Ro R