

**MITOPENCOURSEWARE**  
MASSACHUSETTS INSTITUTE OF TECHNOLOGY

**6.976**

***High Speed Communication Circuits and Systems***

***Lecture 10***


***Mixers***

**Michael Perrott**

**Massachusetts Institute of Technology**

**Copyright © 2003 by Michael H. Perrott**


# Mixer Design for Wireless Systems

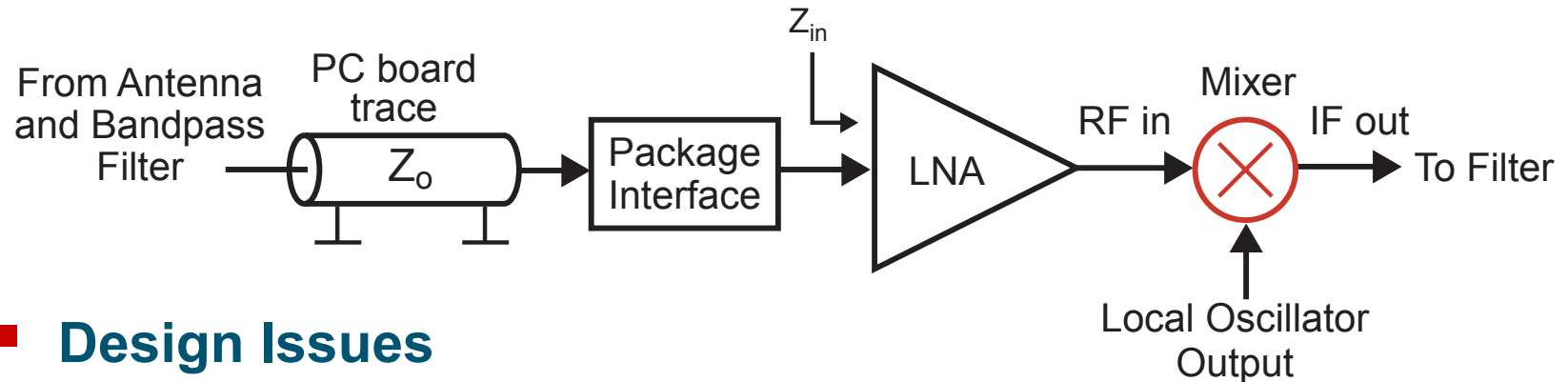

## ■ Design Issues


- Noise Figure – impacts receiver sensitivity
- Linearity (IIP3) – impacts receiver blocking performance
- Conversion gain – lowers noise impact of following stages
- Power match – want max voltage gain rather than power match for integrated designs
- Power – want low power dissipation
- Isolation – want to minimize interaction between the RF, IF, and LO ports
- Sensitivity to process/temp variations – need to make it manufacturable in high volume

# Ideal Mixer Behavior

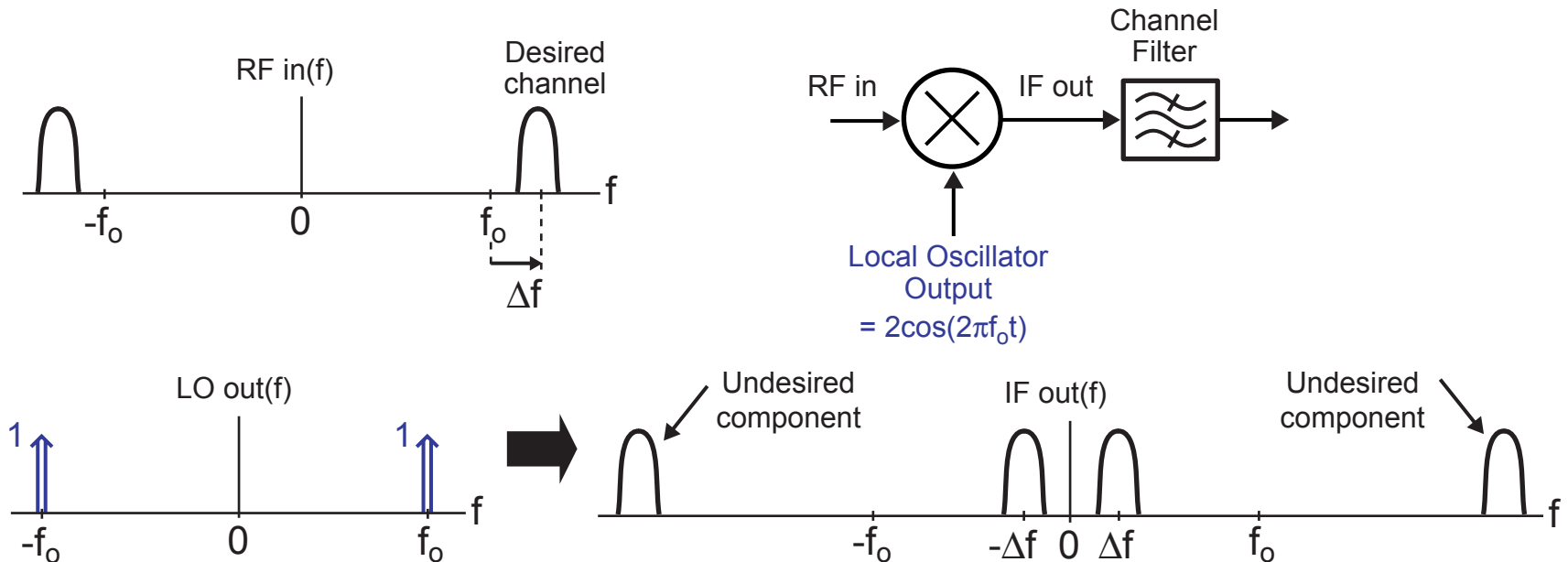


- **RF spectrum converted to a lower IF center frequency**
  - **IF stands for intermediate frequency**
    - If IF frequency is nonzero – heterodyne or low IF receiver
    - If IF frequency is zero – homodyne receiver
- **Use a filter at the IF output to remove undesired high frequency components**

# The Issue of Aliasing

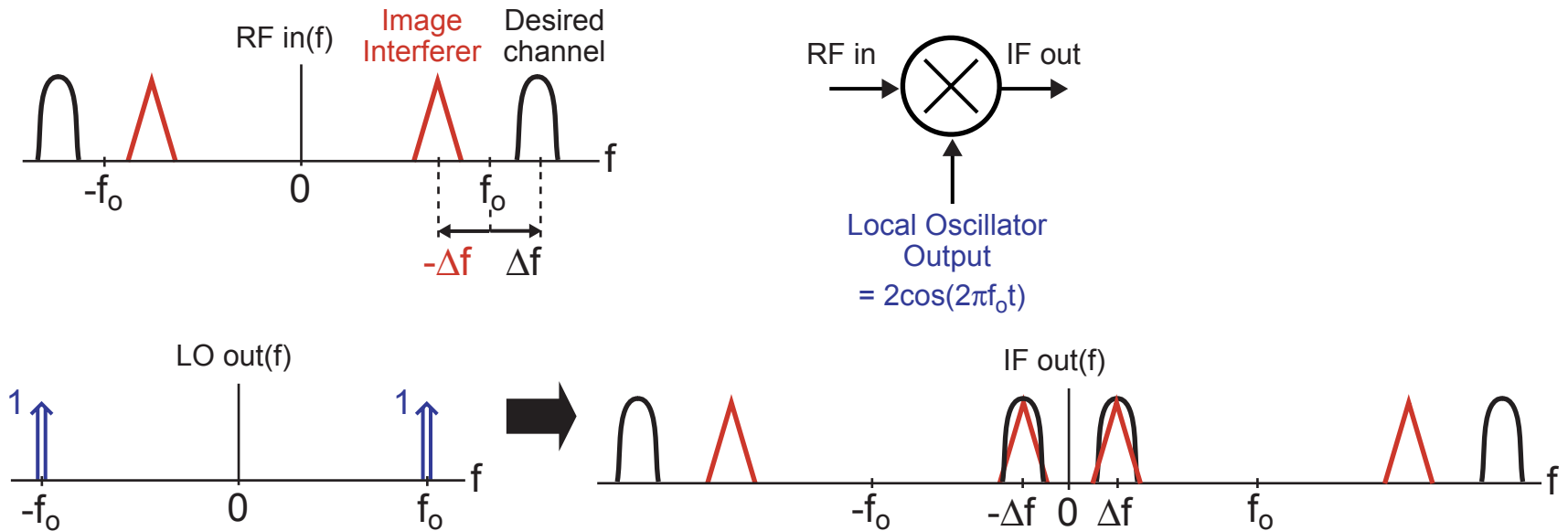


- **When the IF frequency is nonzero, there is an image band for a given desired channel band**
  - Frequency content in image band will combine with that of the desired channel at the IF output
  - The impact of the image interference cannot be removed through filtering at the IF output!

# LO Feedthrough

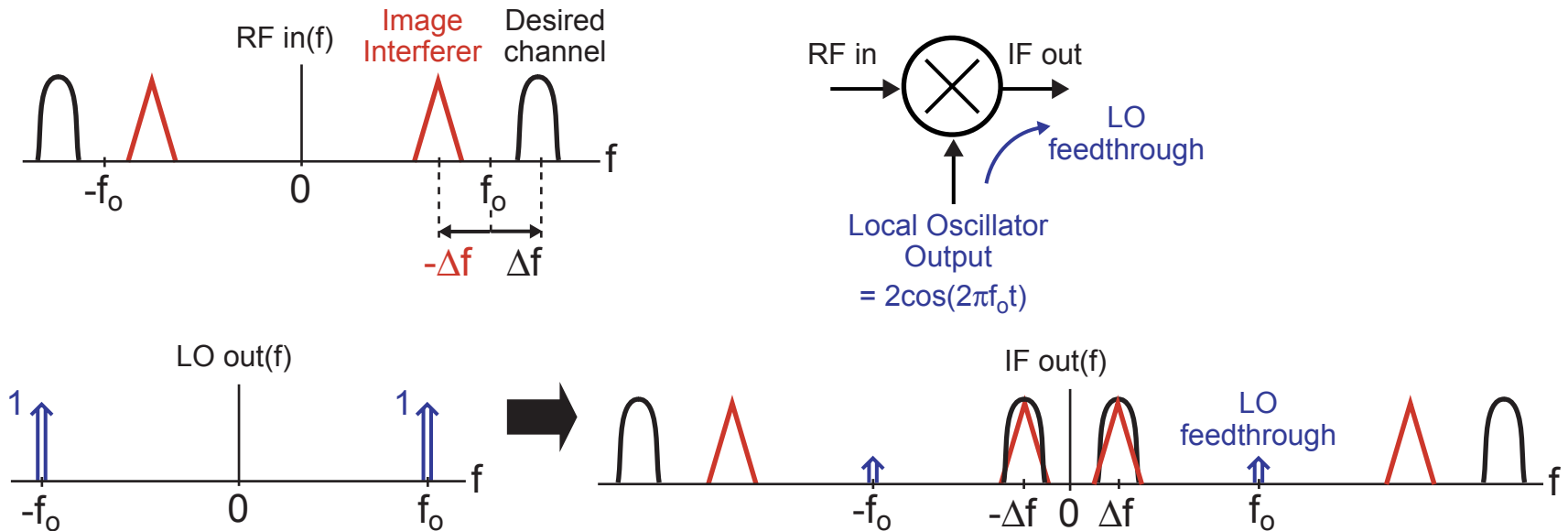


- **LO feedthrough will occur from the LO port to IF output port due to parasitic capacitance, power supply coupling, etc.**
  - Often significant since LO output much higher than RF signal
    - If large, can potentially desensitize the receiver due to the extra dynamic range consumed at the IF output
    - If small, can generally be removed by filter at IF output

# Reverse LO Feedthrough

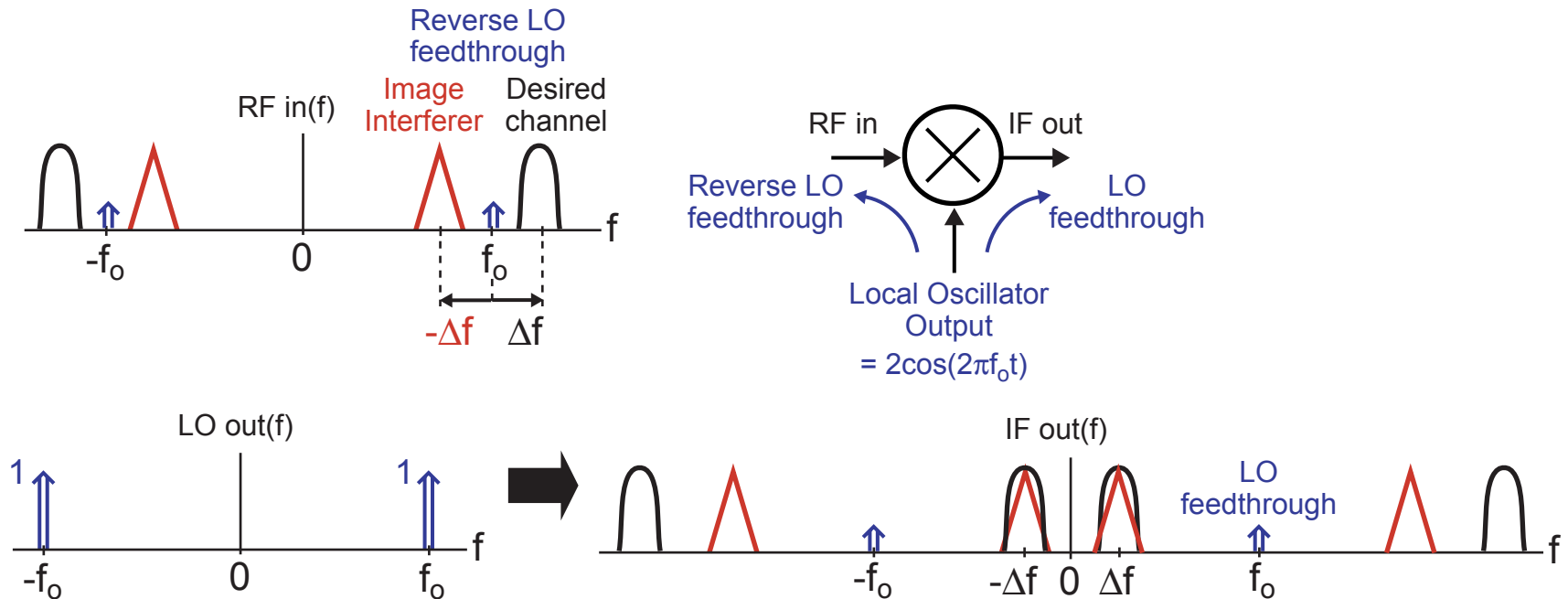


- Reverse LO feedthrough will occur from the LO port to RF input port due to parasitic capacitance, etc.
  - If large, and LNA doesn't provide adequate isolation, then LO energy can leak out of antenna and violate emission standards for radio
  - Must insure that isolate to antenna is adequate

# Self-Mixing of Reverse LO Feedthrough

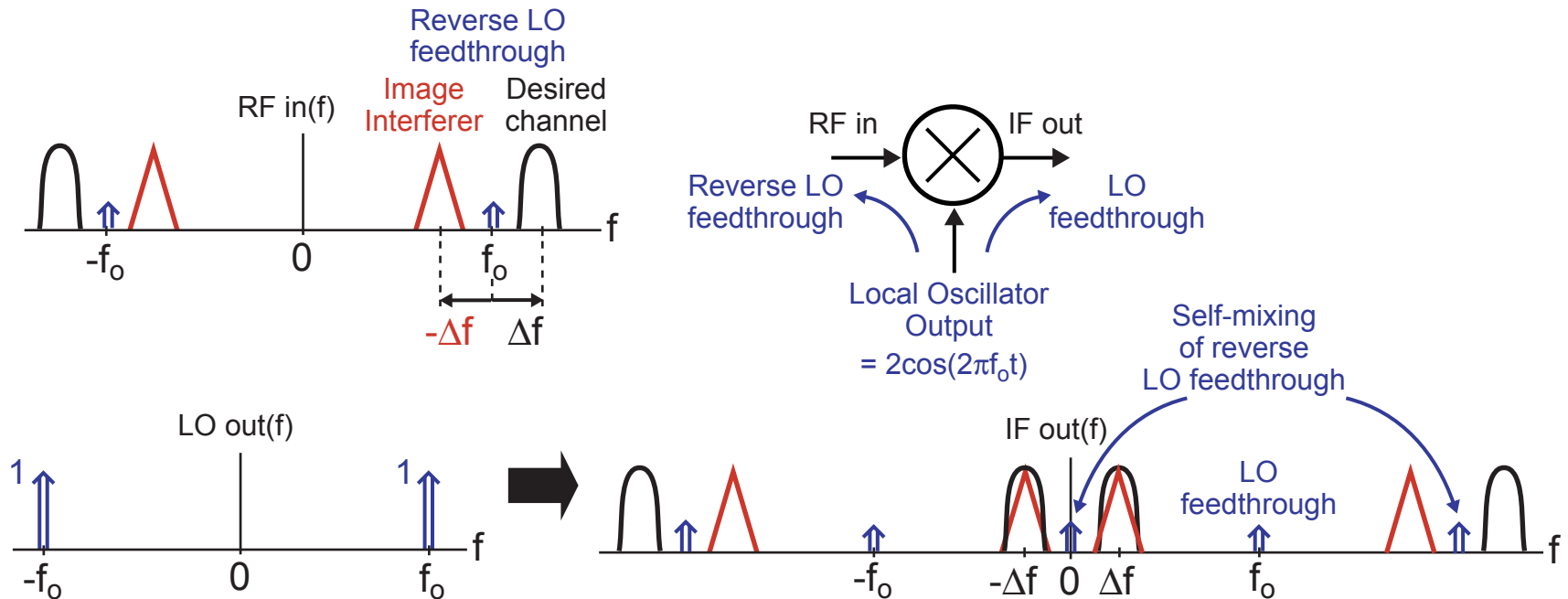

- **LO component in the RF input can pass back through the mixer and be modulated by the LO signal**
  - **DC and  $2f_0$  component created at IF output**
  - **Of no consequence for a heterodyne system, but can cause problems for homodyne systems (i.e., zero IF)**

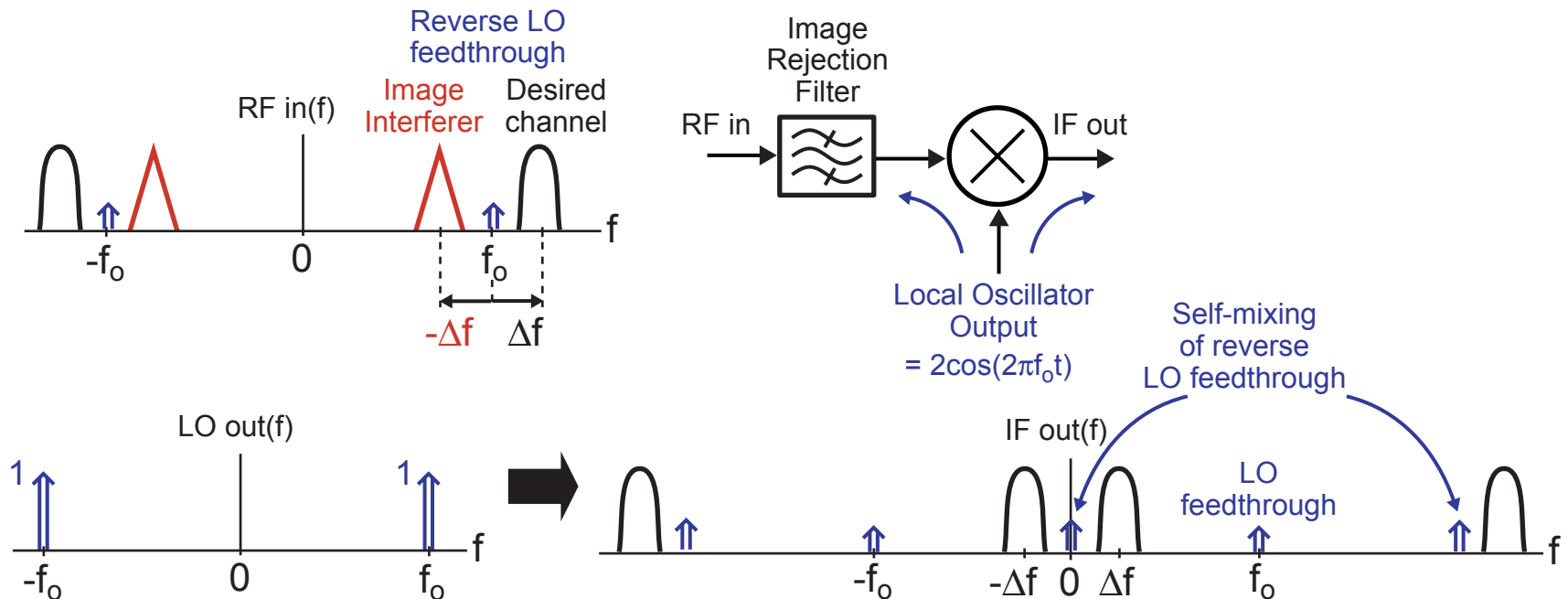
# Removal of Image Interference – Solution 1



- An image reject filter can be used *before* the mixer to prevent the image content from aliasing into the desired channel at the IF output
- Issue – must have a high IF frequency
  - Filter bandwidth must be large enough to pass all channels
  - Filter Q cannot be arbitrarily large (low IF requires high Q)



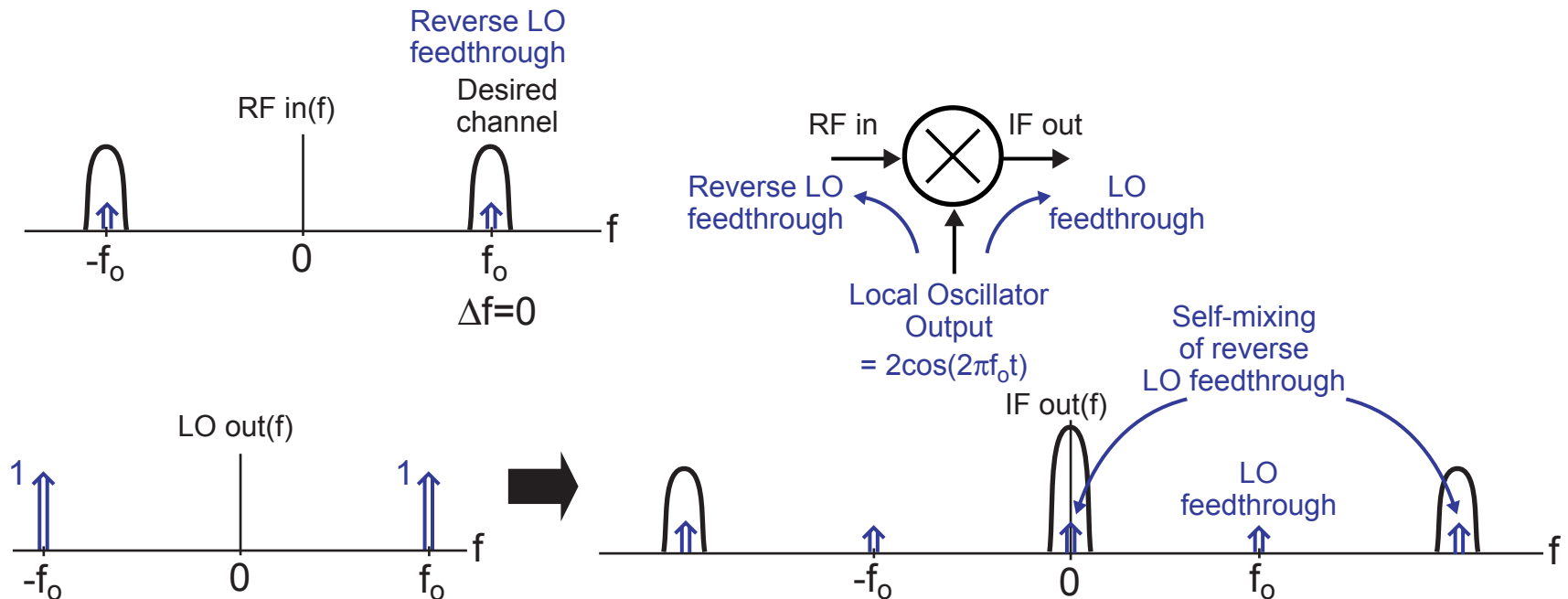
# Removal of Image Interference – Solution 2



- **Mix directly down to baseband (i.e., homodyne approach)**
  - With an IF frequency of zero, there is no image band
- **Issues – many!**
  - DC term of LO feedthrough can corrupt signal if time-varying
  - DC offsets can swamp out dynamic range at IF output
  - $1/f$  noise, back radiation through antenna
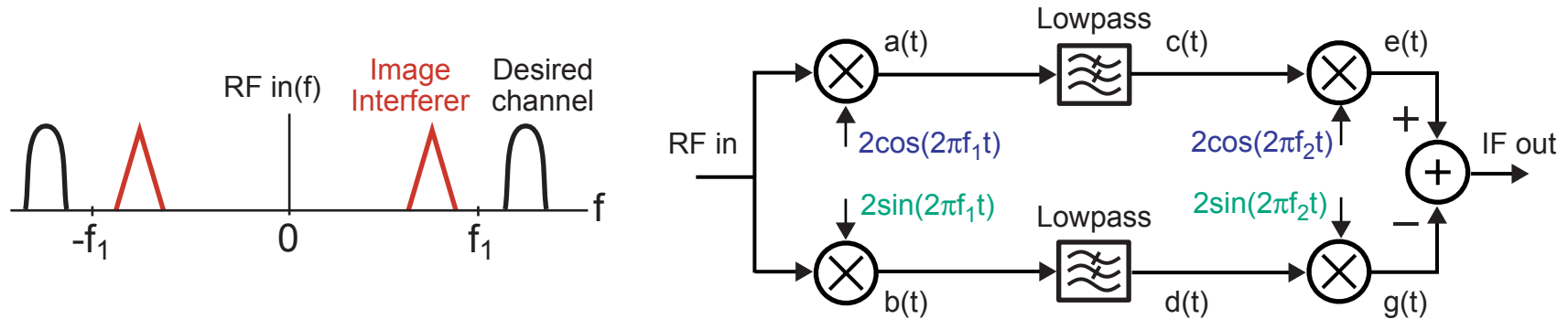
# Removal of Image Interference – Solution 3



- Rather than filtering out the image, we can cancel it out using an image rejection mixer


- Advantages

- Allows a low IF frequency to be used without requiring a high Q filter
- Very amenable to integration


- Disadvantage

- Level of image rejection is determined by mismatch in gain and phase of the top and bottom paths
- Practical architectures limited to 40-50 dB image rejection




# Image Reject Mixer Principles – Step 1

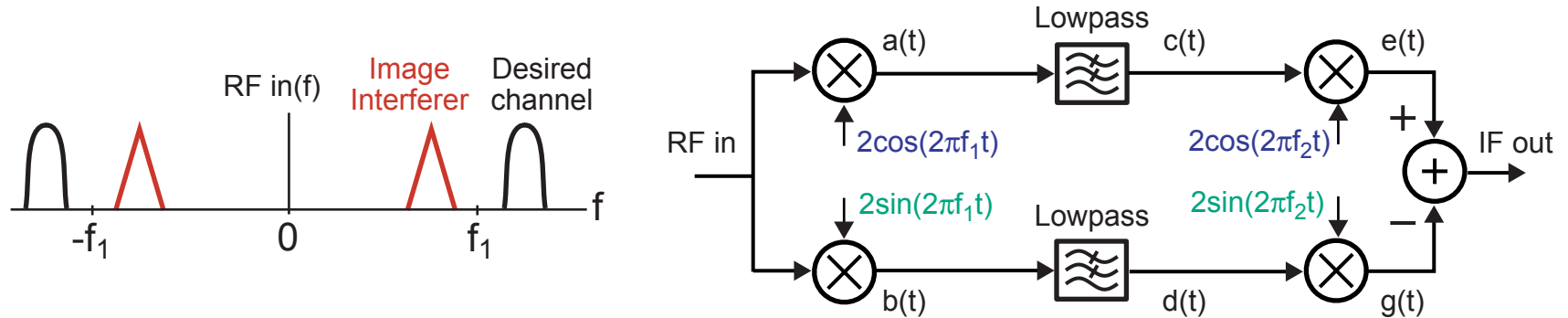

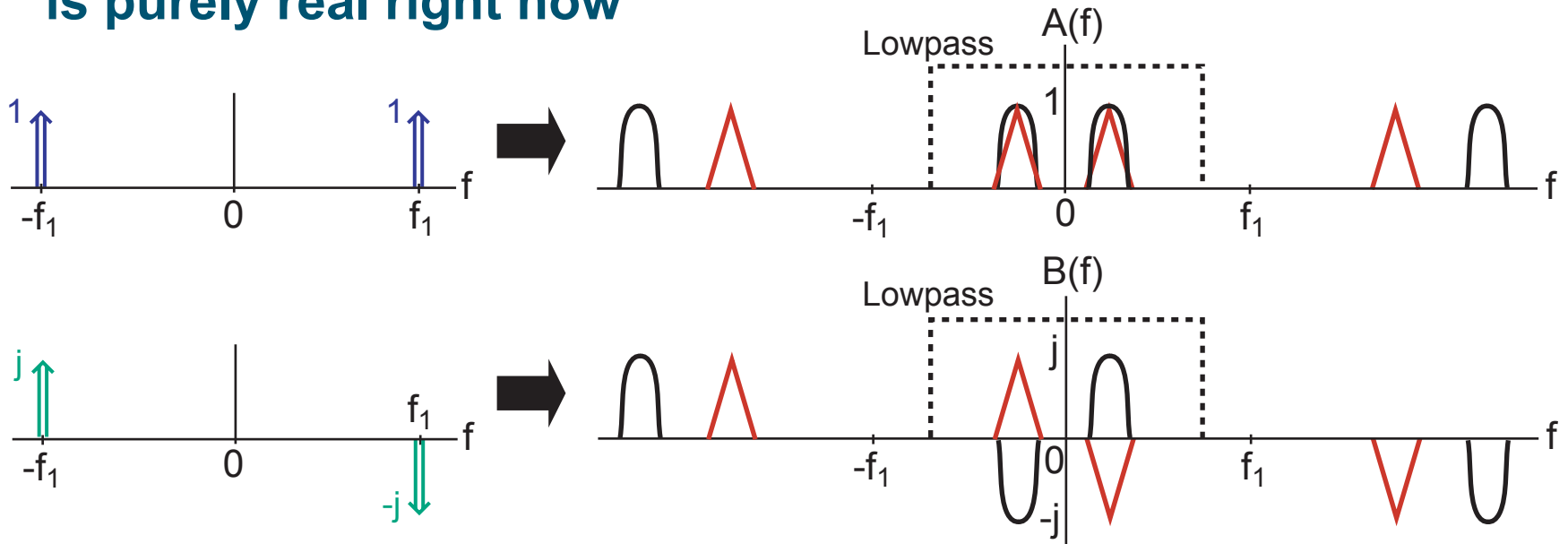
- Note: we are assuming RF in( $f$ ) is purely real right now




# Image Reject Mixer Principles – Step 2

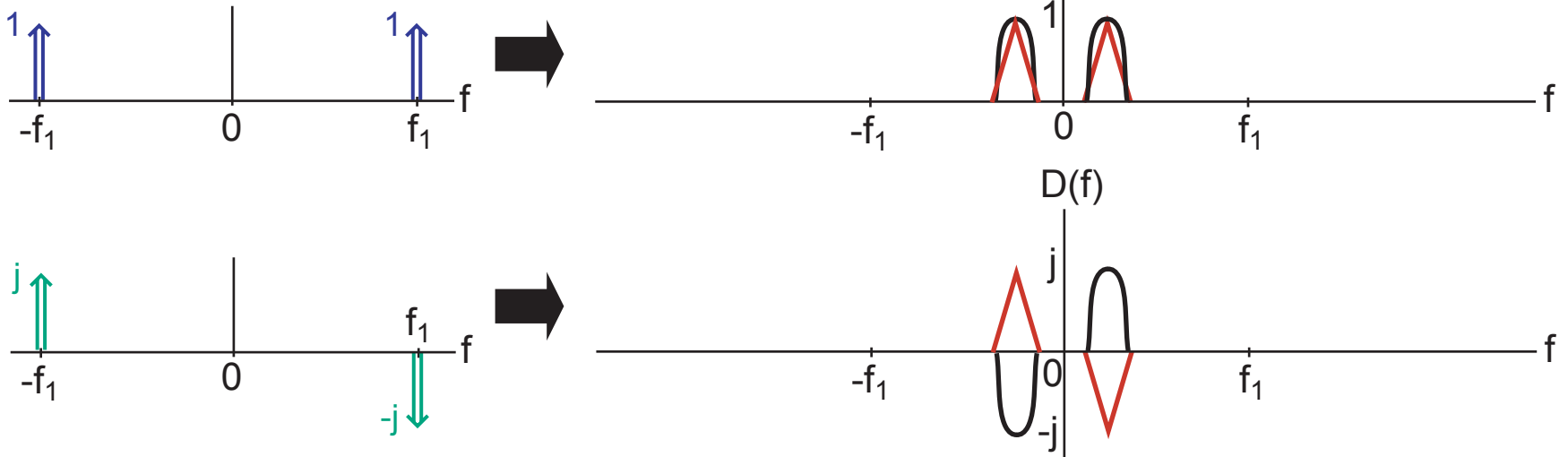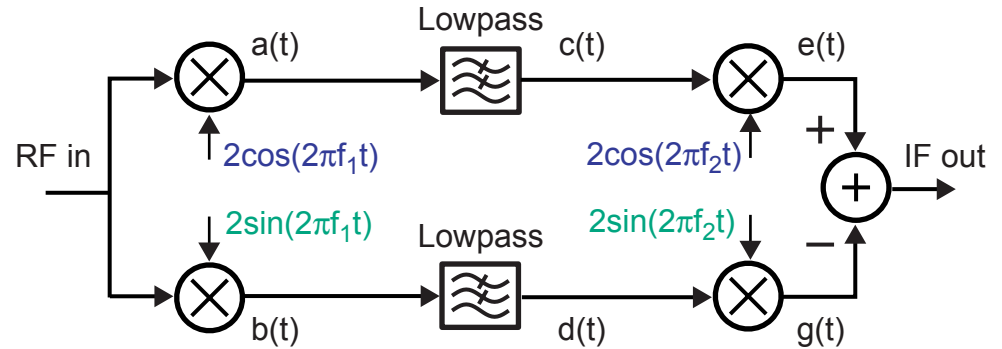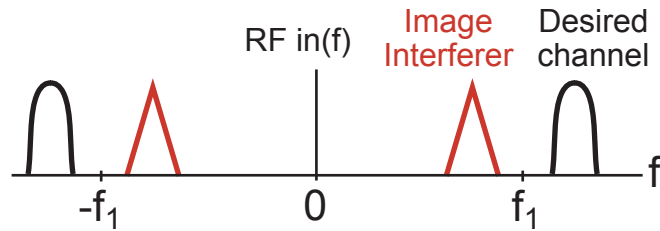


# Image Reject Mixer Principles – Step 3

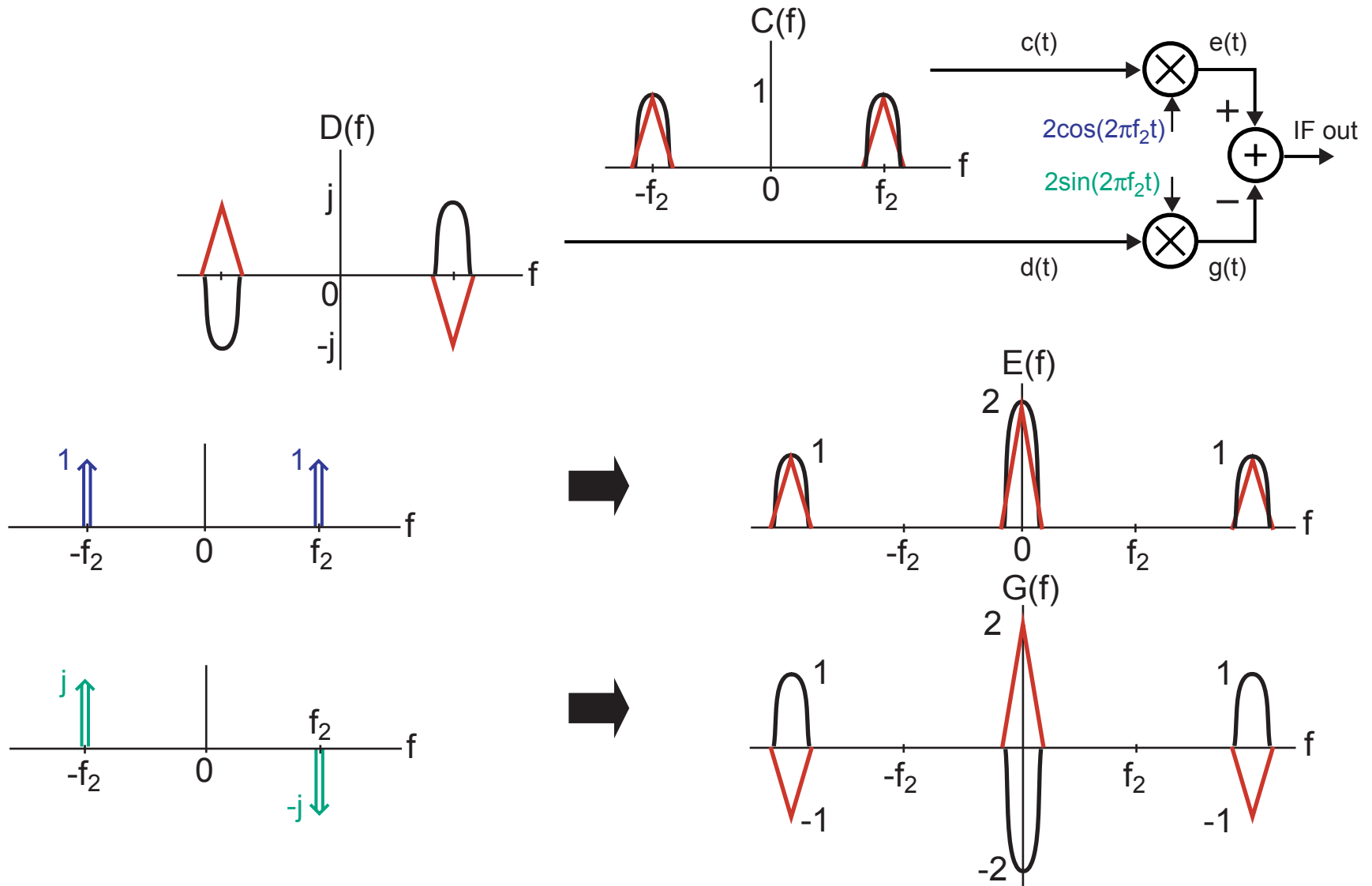

# Image Reject Mixer Principles – Step 4

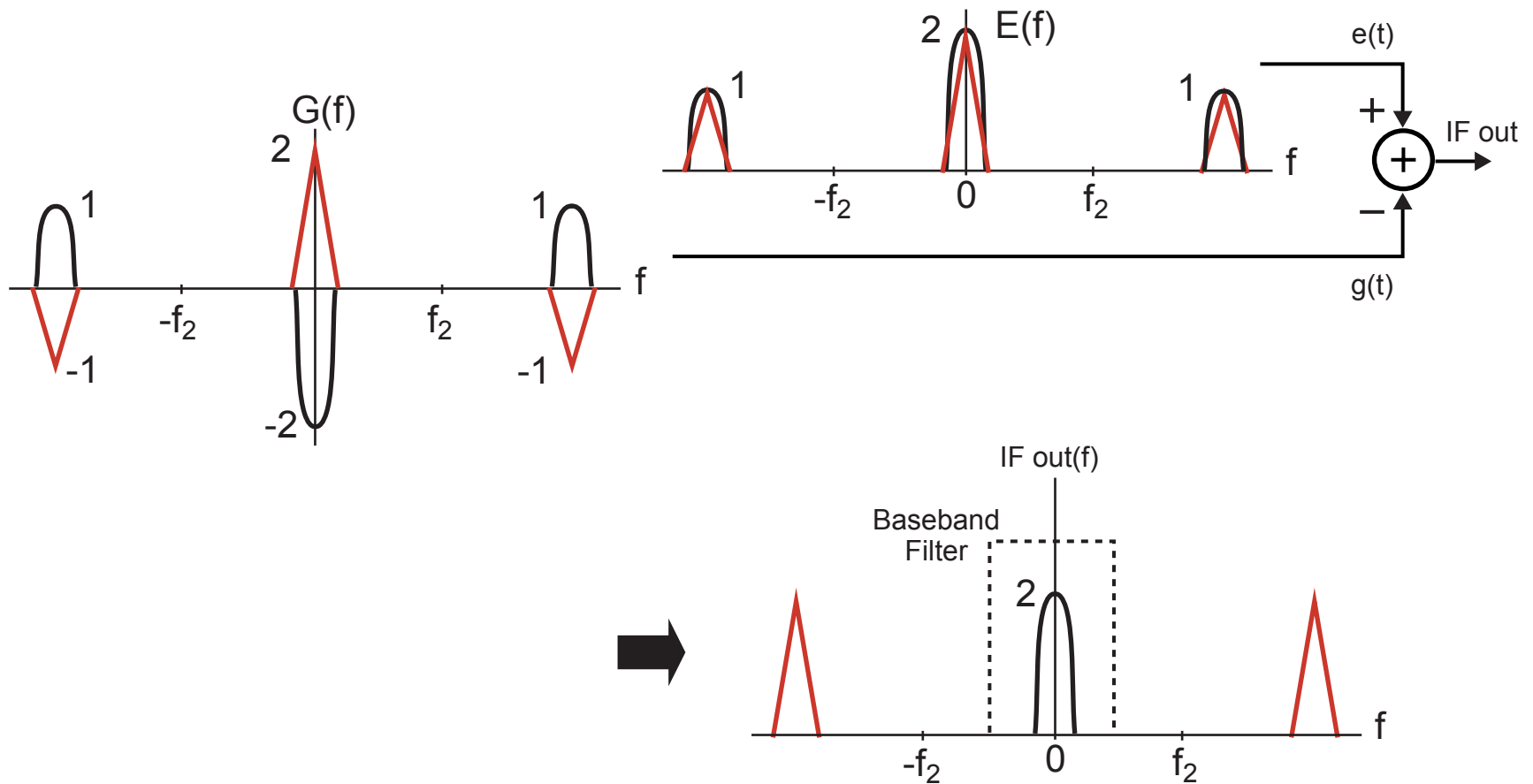

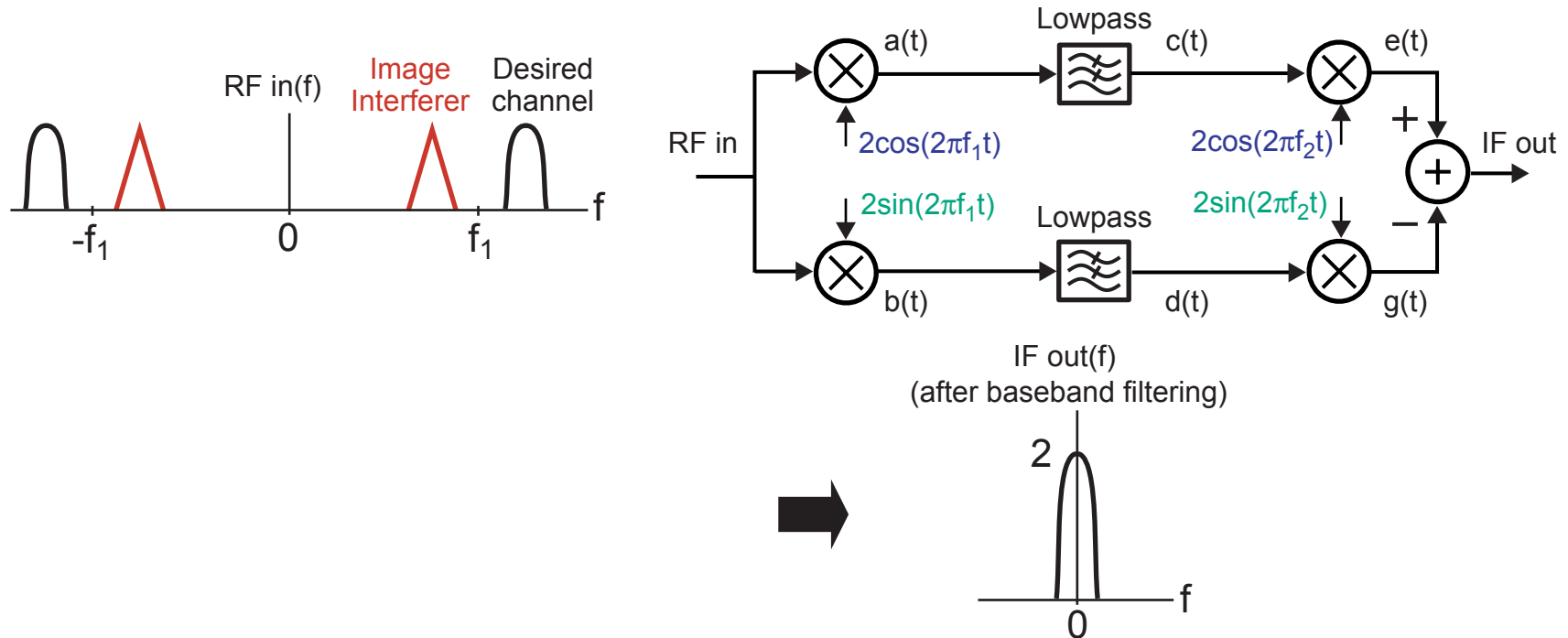
# Image Reject Mixer Principles – Implementation Issues



- For all analog architecture, going to zero IF introduces sensitivity to  $1/f$  noise at IF output
  - Can fix this problem by digitizing  $c(t)$  and  $d(t)$ , and then performing final mixing in the digital domain
- Can generate accurate quadrature sine wave signals by using a frequency divider


## What if RF in(f) is Purely Imaginary?

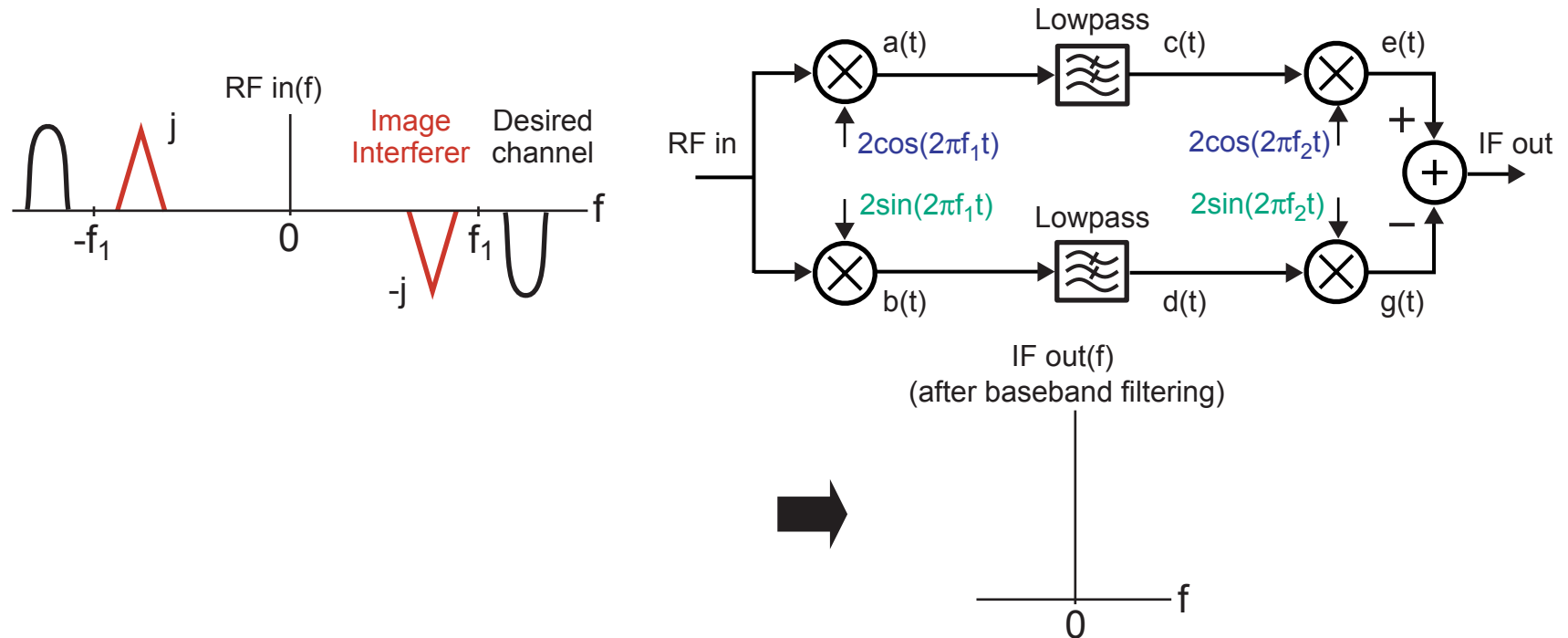

- **Both desired and image signals disappear!**
  - Architecture is sensitive to the phase of the RF input
- **Can we modify the architecture to fix this issue?**




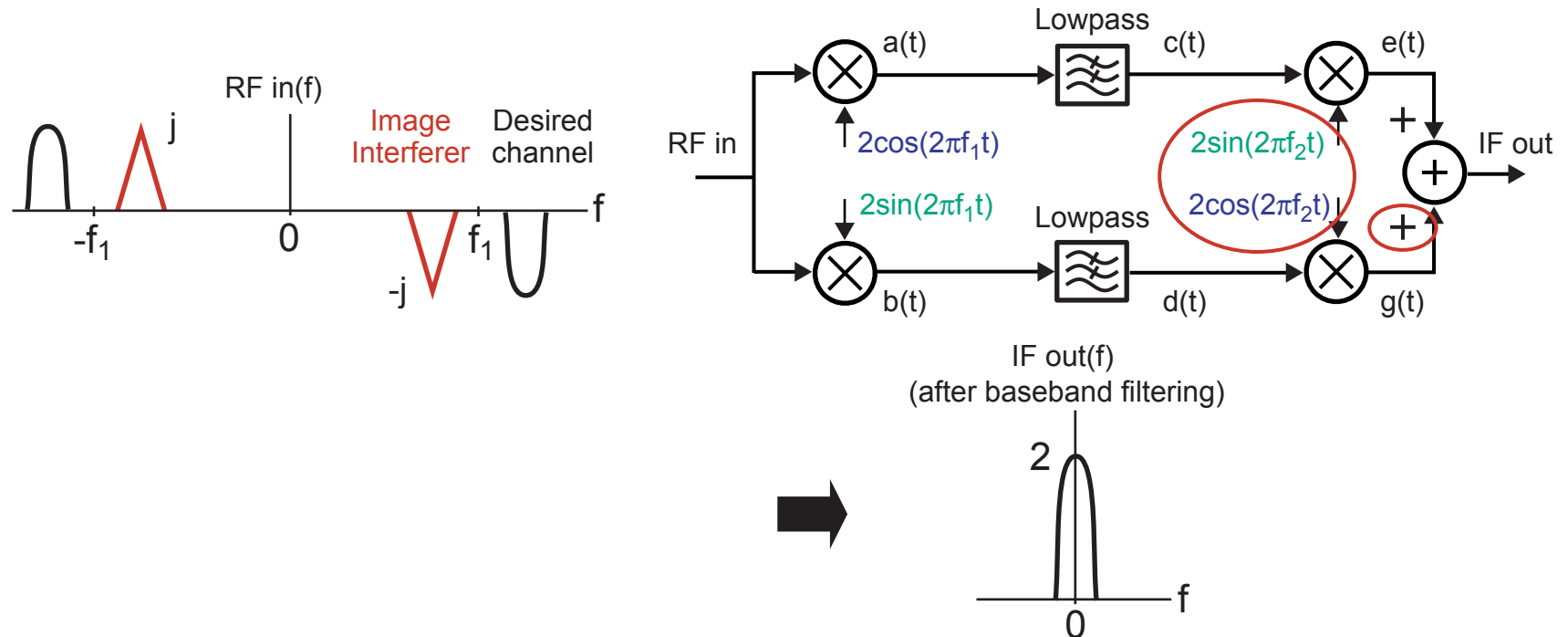
# Modification of Mixer Architecture for Imaginary RF in(f)




- **Desired channel now appears given two changes**
  - Sine and cosine demodulators are switched in second half of image rejection mixer
  - The two paths are now added rather than subtracted
- **Issue – architecture now zeros out desired channel when RF in(f) is purely real**

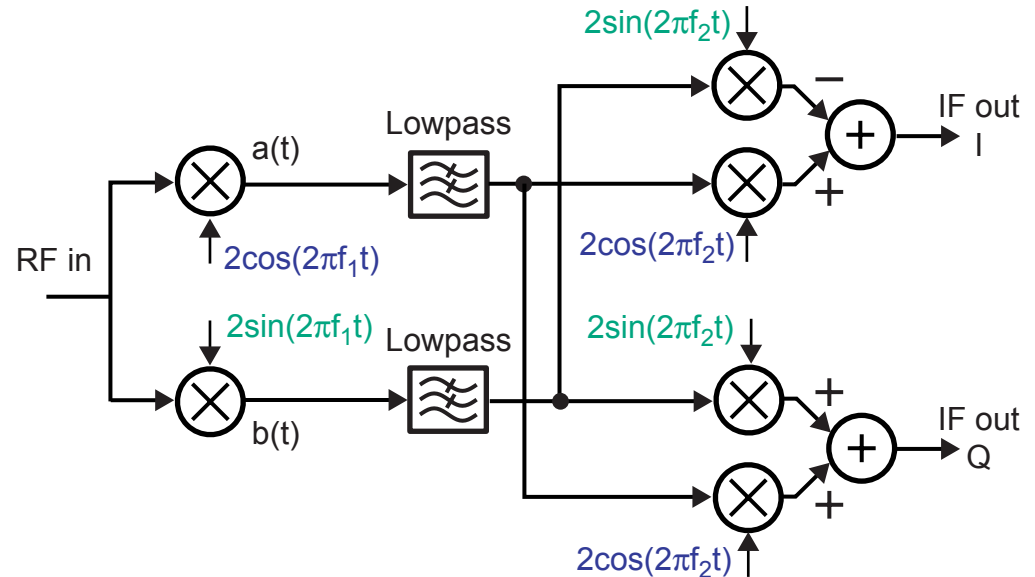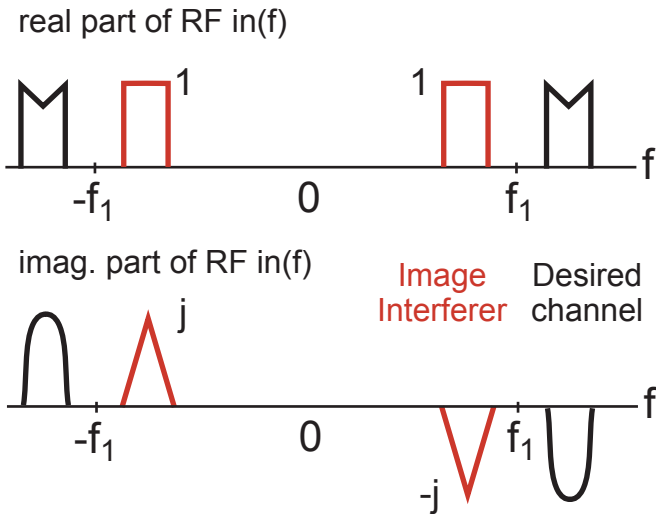
# Overall Mixer Architecture – Use I/Q Demodulation



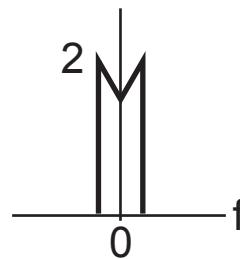IF out(f) (I component)  
(after baseband filtering)




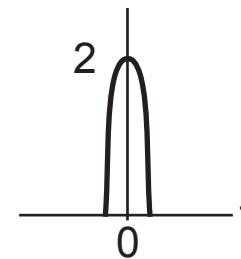IF out(f) (Q component)  
(after baseband filtering)




- Both real and imag. parts of RF input now pass through
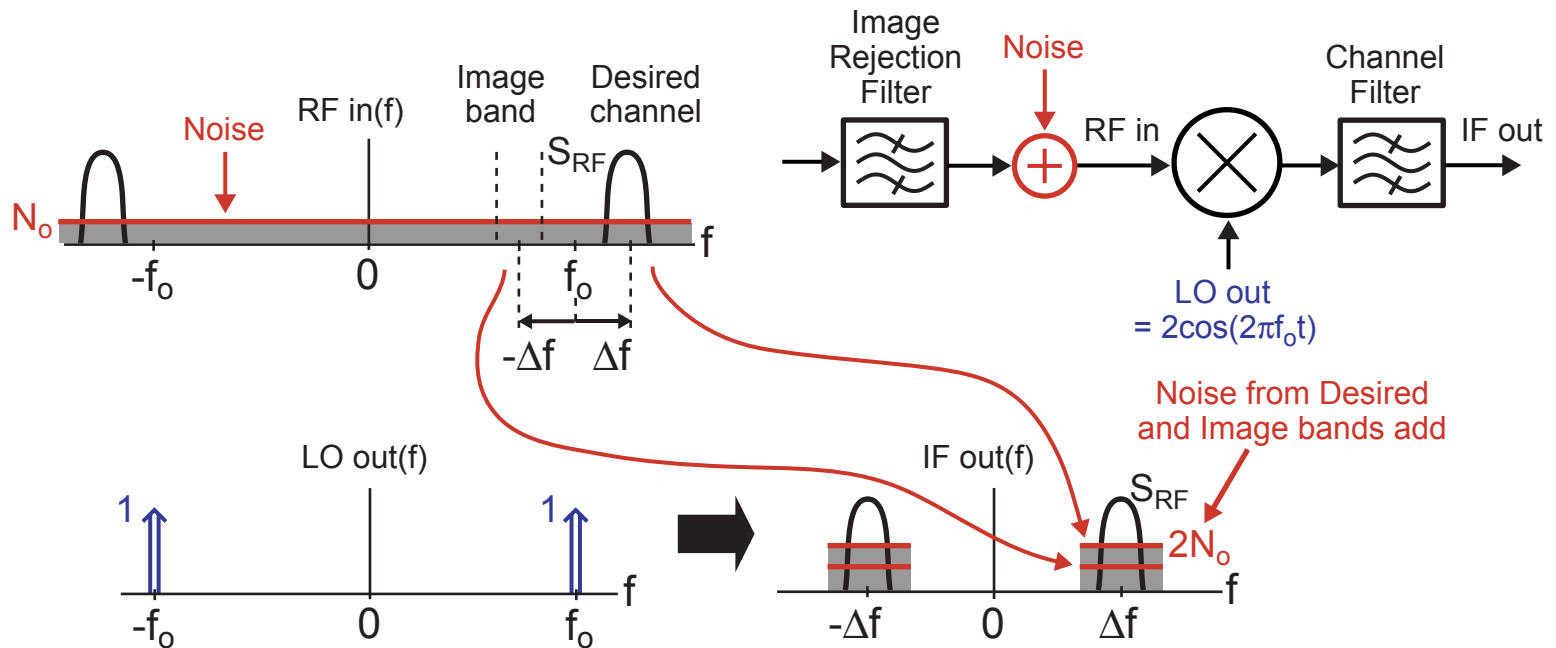
# Mixer Single-Sideband (SSB) Noise Figure




- **Issue – broadband noise from mixer or front end filter will be located in both image and desired bands**
  - Noise from both image and desired bands will combine in desired channel at IF output
    - Channel filter cannot remove this
  - **Mixers are inherently noisy!**
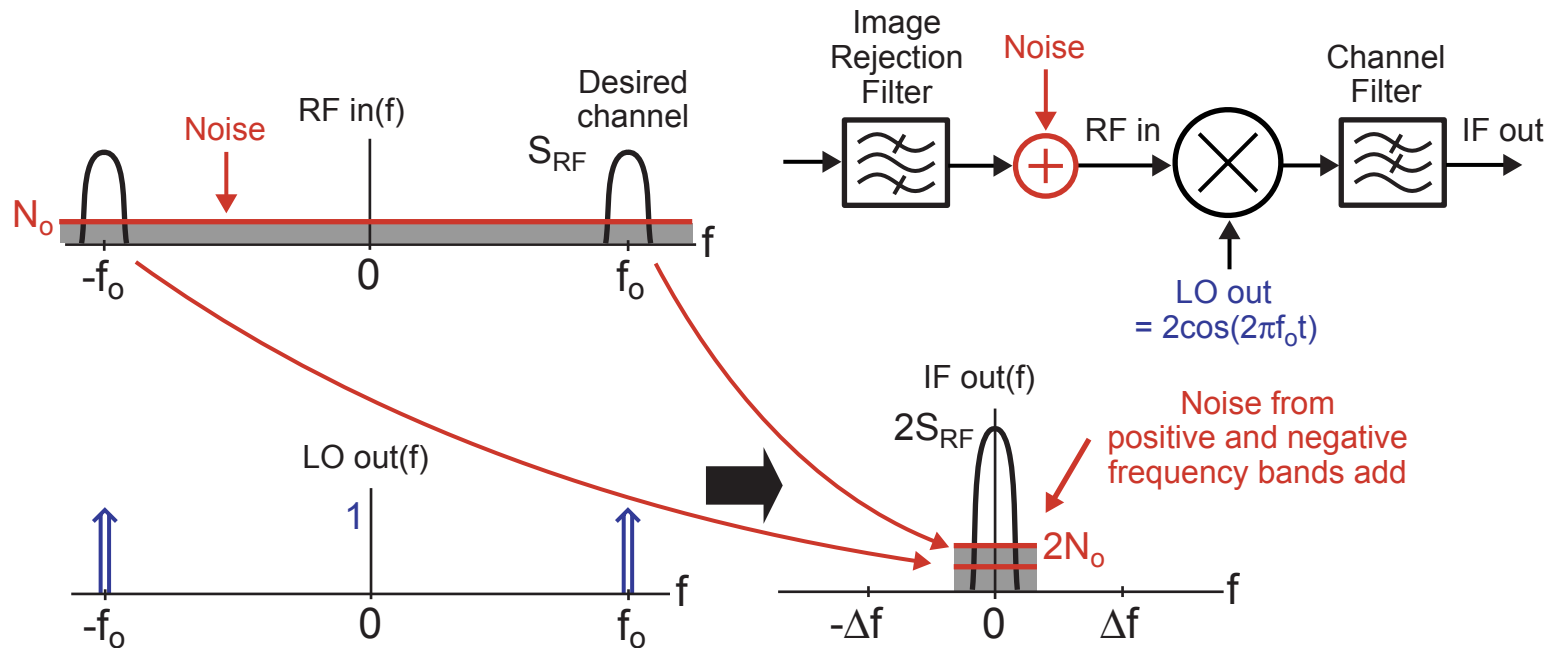
# Mixer Double-Sideband (DSB) Noise Figure



- For zero IF, there is no image band
  - Noise from positive and negative frequencies combine, but the signals do as well
- DSB noise figure is 3 dB lower than SSB noise figure
  - DSB noise figure often quoted since it sounds better
- For either case, Noise Figure computed through simulation

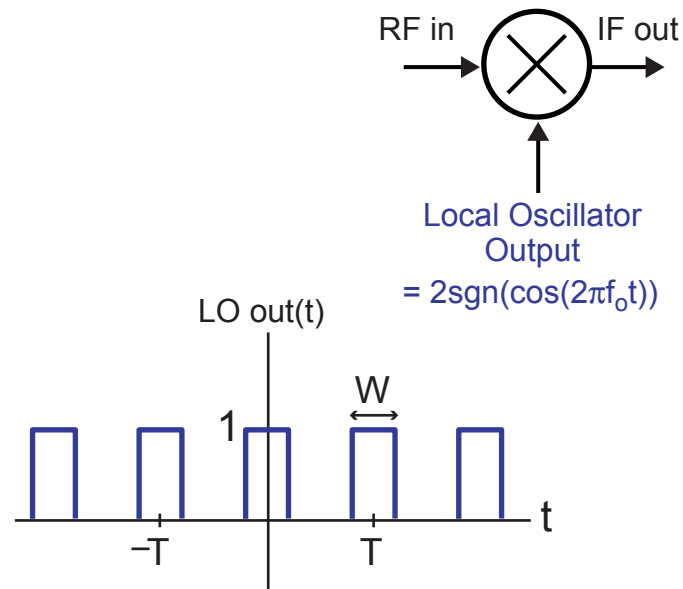
# A Practical Issue – Square Wave LO Oscillator Signals




- **Square waves are easier to generate than sine waves**
  - How do they impact the mixing operation when used as the LO signal?
  - We will briefly review Fourier transforms (series) to understand this issue
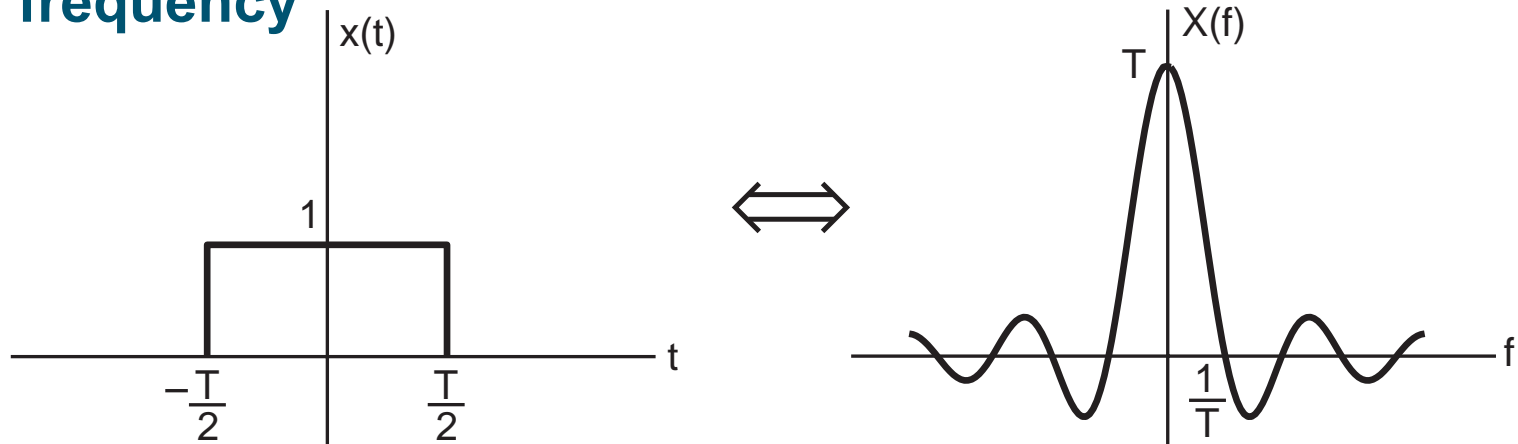
## Two Important Transform Pairs

- Transform of a rectangle pulse in time is a sinc function in frequency




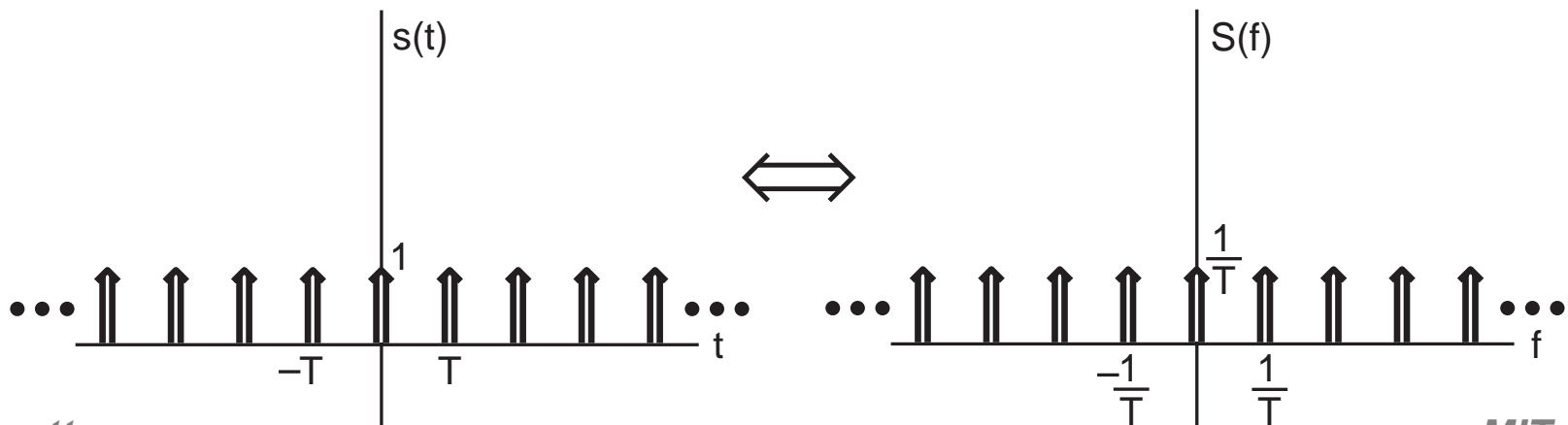- Transform of an impulse train in time is an impulse train in frequency



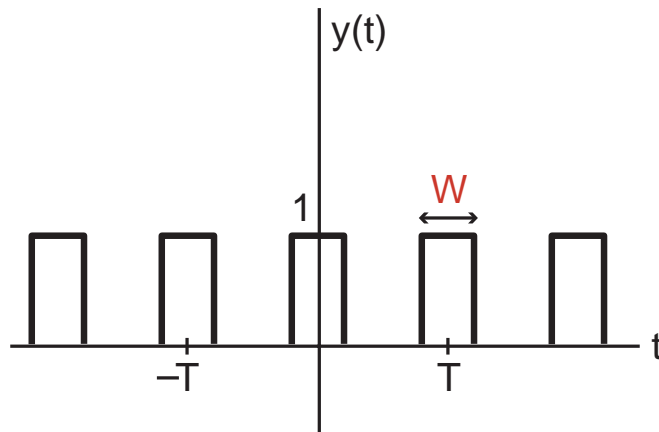
# Decomposition of Square Wave to Simplify Analysis


- Consider now a square wave with duty cycle  $W/T$



- Decomposition in time

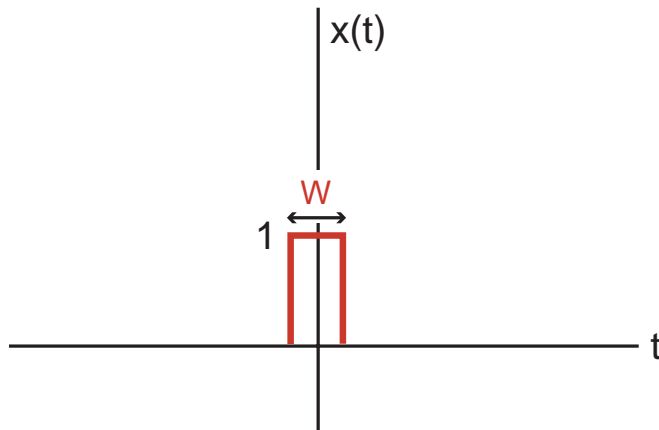


\*

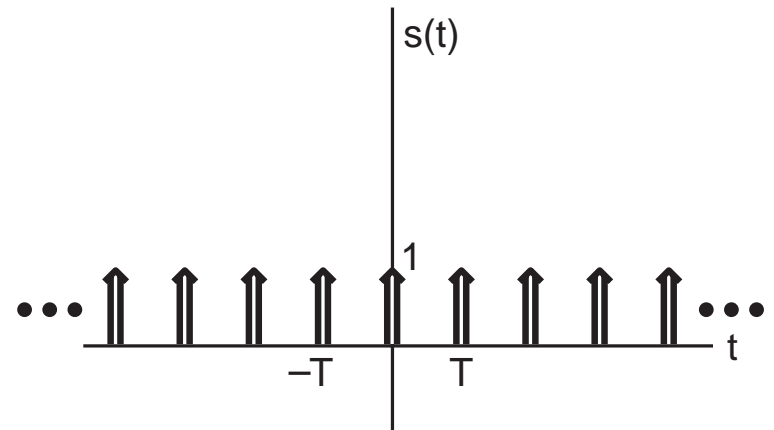

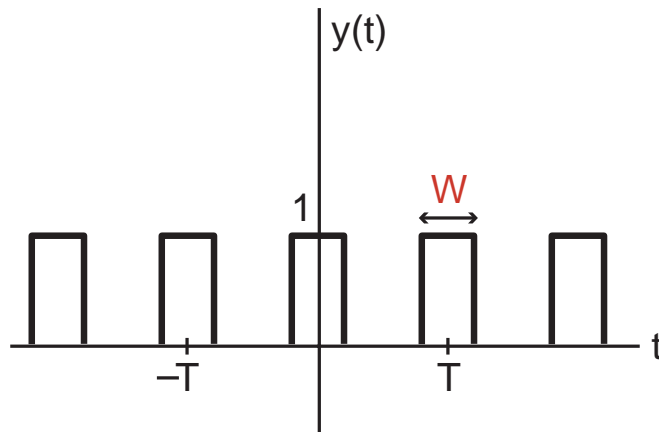
# Associated Frequency Transforms


- Consider now a square wave with duty cycle  $W/T$



- Decomposition in frequency

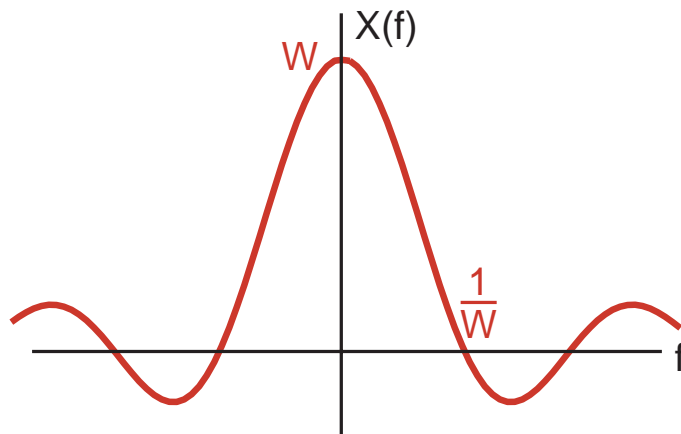


×

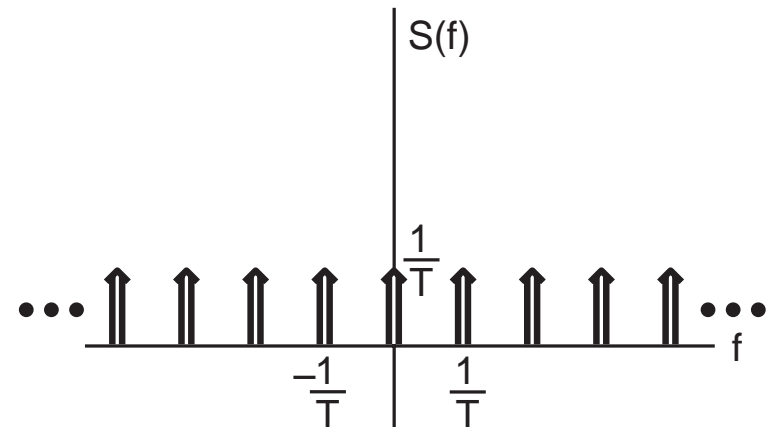




# Overall Frequency Transform of a Square Wave

- Resulting transform relationship

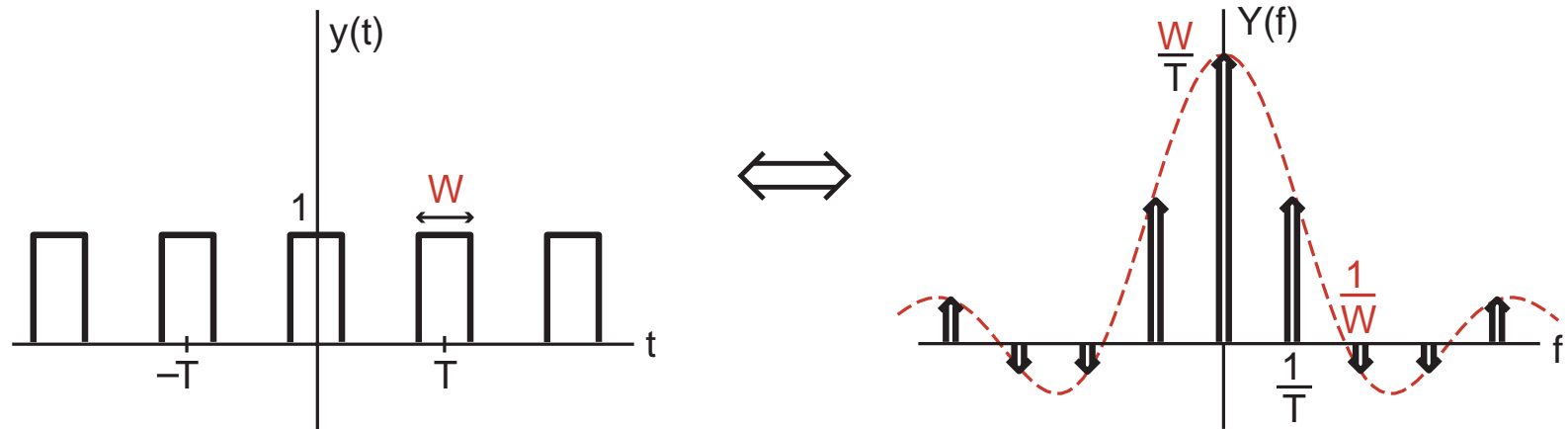


- Fundamental at frequency  $1/T$ 
  - Higher harmonics have lower magnitude
- If  $W = T/2$  (i.e., 50% duty cycle)
  - No even harmonics!
- If amplitude varies between 1 and -1 (rather than 1 and 0)
  - No DC component
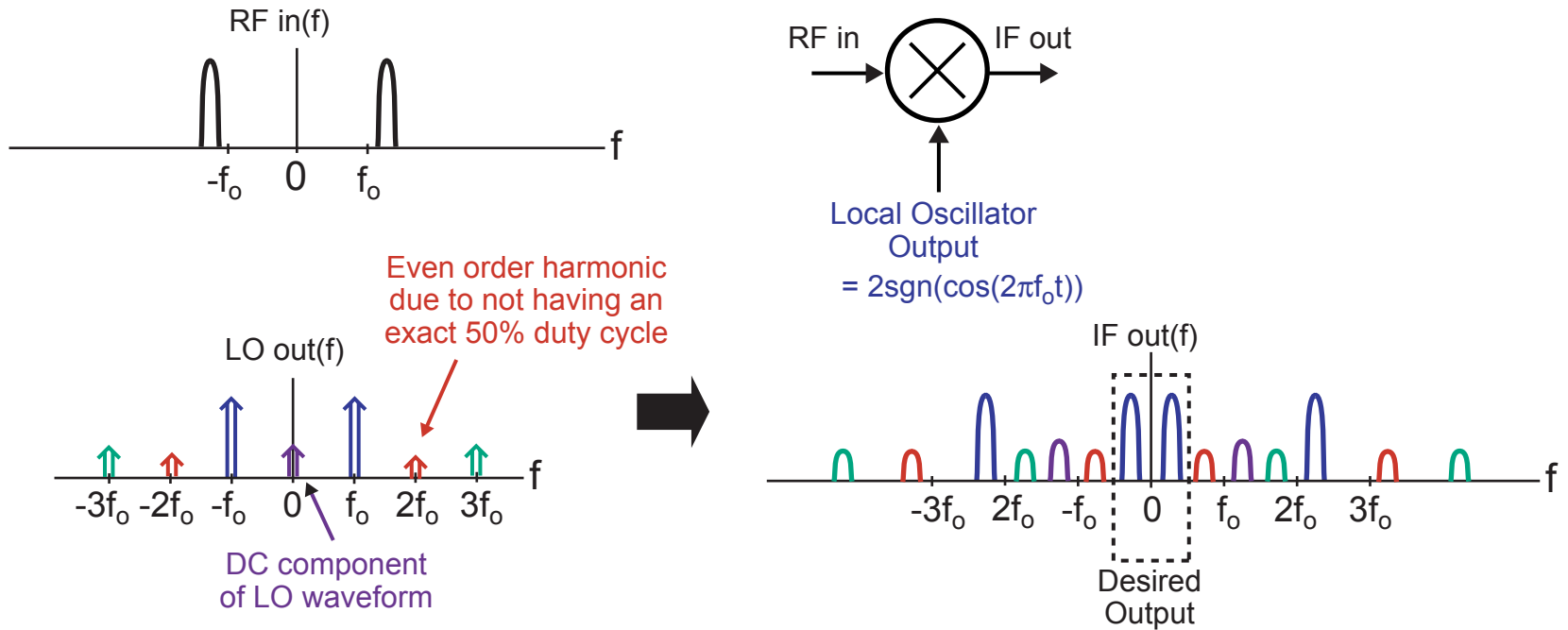
# Analysis of Using Square-Wave for LO Signal



- Each frequency component of LO signal will now mix with the RF input
  - If RF input spectrum sufficiently narrowband with respect to  $f_0$ , then no aliasing will occur
- Desired output (mixed by the fundamental component) can be extracted using a filter at the IF output

# Voltage Conversion Gain

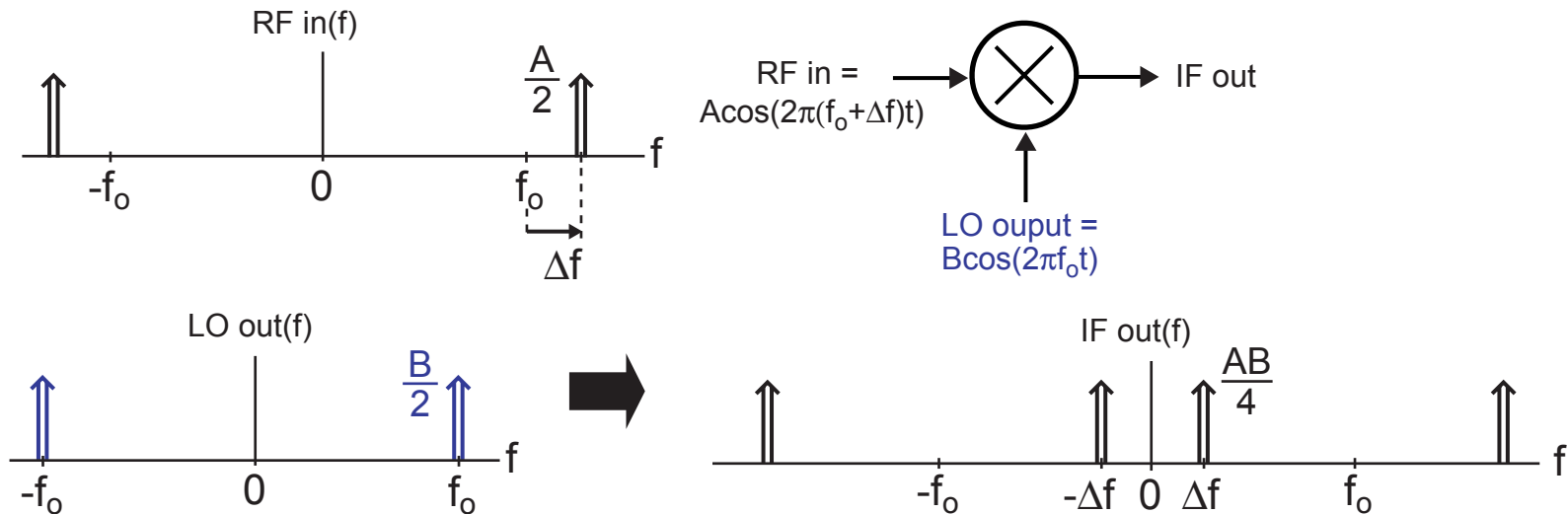


- Defined as voltage ratio of desired IF value to RF input
- Example: for an ideal mixer with RF input =  $A \sin(2\pi(f_0 + \Delta f)t)$  and sine wave LO signal =  $B \cos(2\pi f_0 t)$

$$IF \text{ out}(t) = \frac{AB}{2} \left( \cos(2\pi(\Delta f)t) + \cos(2\pi(2f_0 + \Delta f)t) \right)$$

$$\Rightarrow \text{Voltage Conversion Gain} = \frac{AB/2}{A} = \frac{B}{2}$$


- For practical mixers, value depends on mixer topology and LO signal (i.e., sine or square wave)

# Impact of High Voltage Conversion Gain

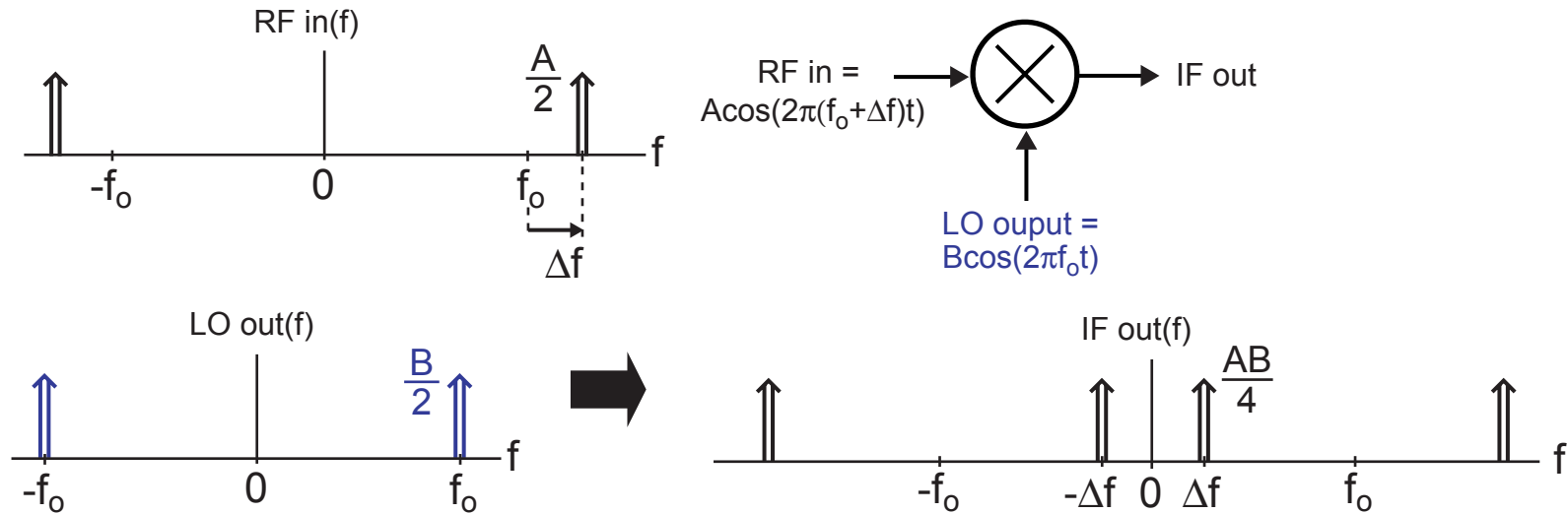


- **Benefit of high voltage gain**
  - The noise of later stages will have less of an impact
- **Issues with high voltage gain**
  - May be accompanied by higher noise figure than could be achieved with lower voltage gain
  - May be accompanied by nonlinearities that limit interference rejection (i.e., passive mixers can generally be made more linear than active ones)

# Impact of Nonlinearity in Mixers

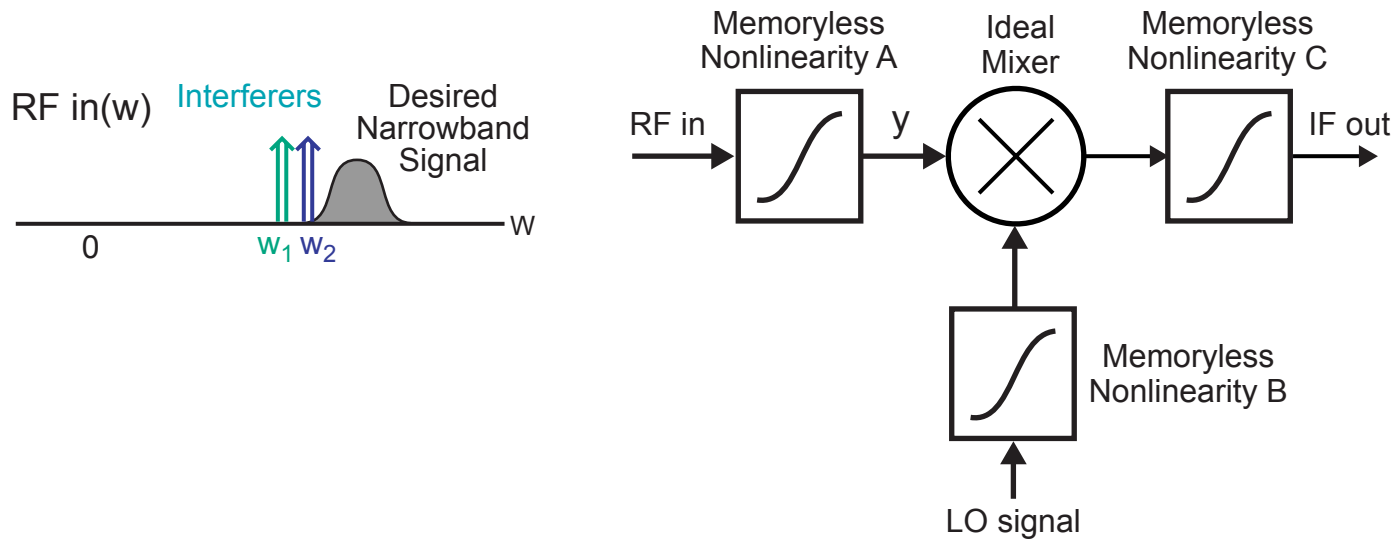


- Ignoring dynamic effects, we can model mixer as nonlinearities around an ideal mixer
  - Nonlinearity A will have the same impact as LNA nonlinearity (measured with IIP3)
  - Nonlinearity B will change the spectrum of the LO signal
    - Causes additional mixing that must be analyzed
    - Changes conversion gain somewhat
  - Nonlinearity C will cause self mixing of IF output
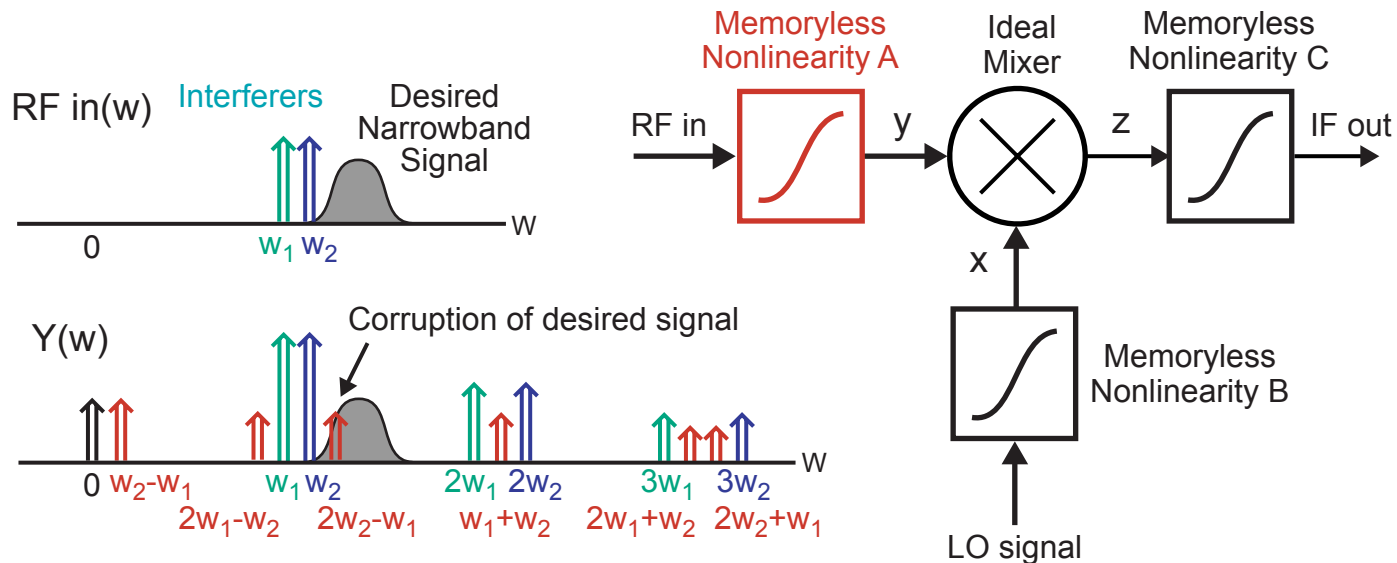
# Primary Focus is Typically Nonlinearity in RF Input Path



- **Nonlinearity B not detrimental in most cases**
  - LO signal often a square wave anyway
- **Nonlinearity C can be avoided by using a linear load (such as a resistor)**
- **Nonlinearity A can hamper rejection of interferers**
  - Characterize with IIP3 as with LNA designs
  - Use two-tone test to measure (similar to LNA)


# The Issue of Balance in Mixers

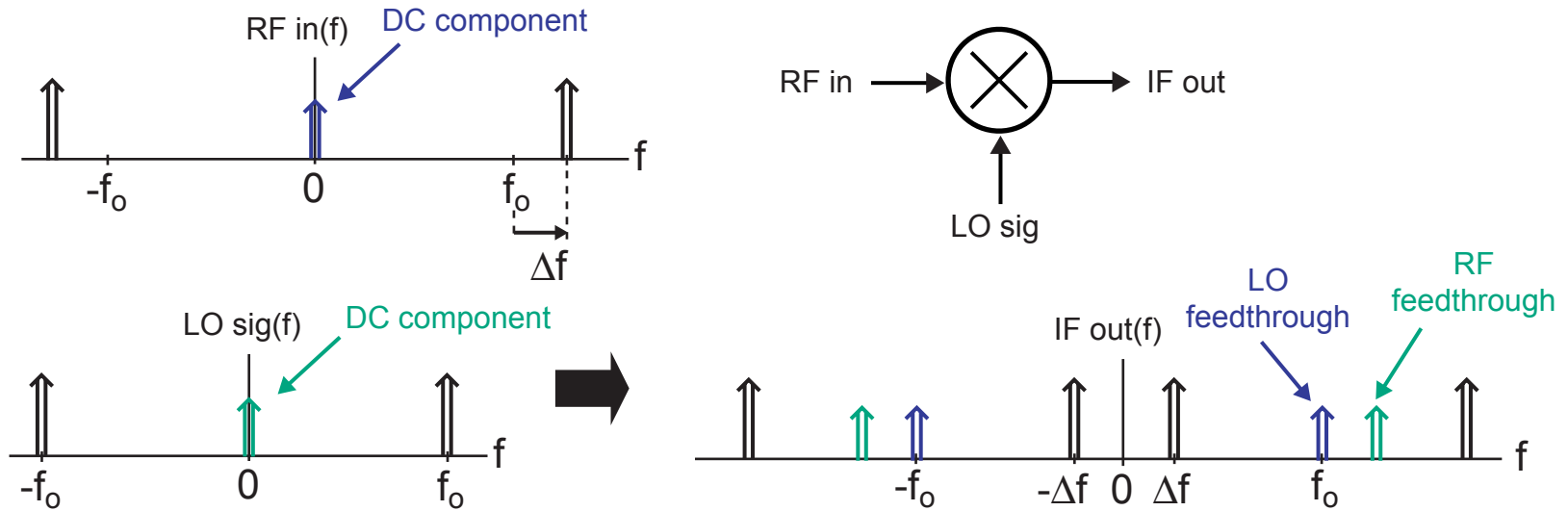

- A balanced signal is defined to have a zero DC component
- Mixers have two signals of concern with respect to this issue – LO and RF signals
  - Unbalanced RF input causes LO feedthrough
  - Unbalanced LO signal causes RF feedthrough
- Issue – transistors require a DC offset
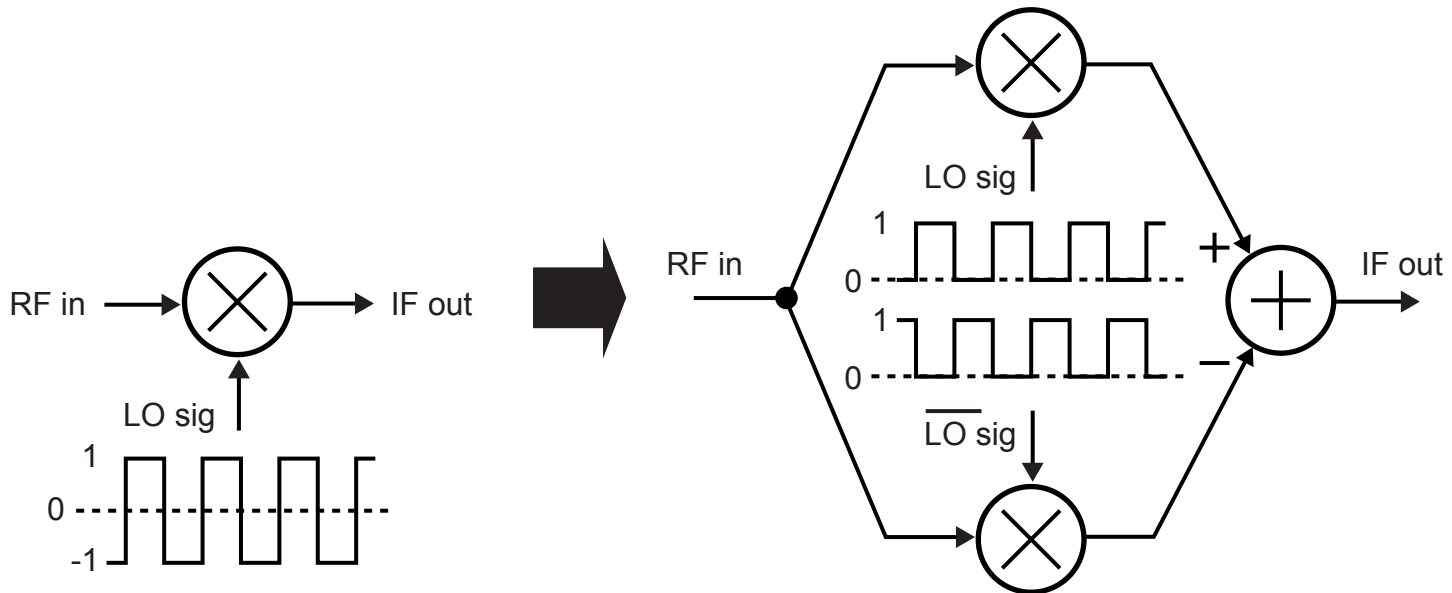
# Achieving a Balanced LO Signal with DC Biasing

- Combine two mixer paths with LO signal 180 degrees out of phase between the paths




- DC component is cancelled





# Transconductor Implementation 1


---

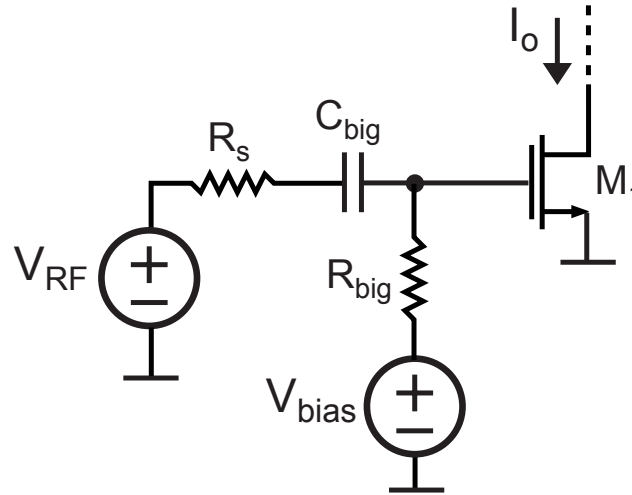

- Apply RF signal to input of common source amp
  - Transistor assumed to be in saturation
  - Transconductance value is the same as that of the transistor
- High  $V_{bias}$  places device in velocity saturation
  - Allows high linearity to be achieved

## Transconductor Implementation 2


---

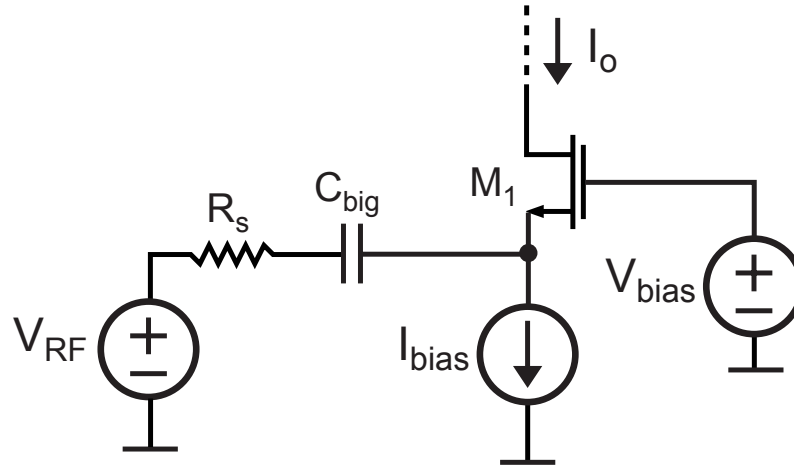

- Apply RF signal to a common gate amplifier
- Transconductance value set by inverse of series combination of  $R_s$  and  $1/g_m$  of transistor
  - Amplifier is effectively degenerated to achieve higher linearity
- $I_{bias}$  can be set for large current density through device to achieve higher linearity (velocity saturation)


# Transconductor Implementation 3

---

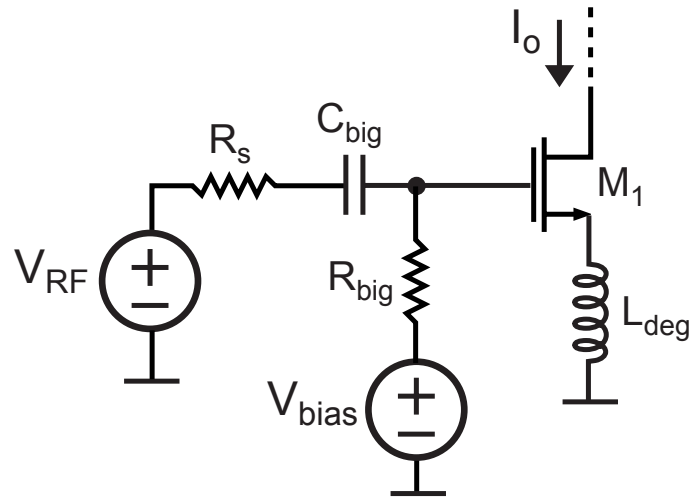


- **Add degeneration to common source amplifier**
  - **Inductor better than resistor**
    - No DC voltage drop
    - Increased impedance at high frequencies helps filter out undesired high frequency components
  - **Don't generally resonate inductor with  $C_{gs}$** 
    - Power match usually not required for IC implementation due to proximity of LNA and mixer
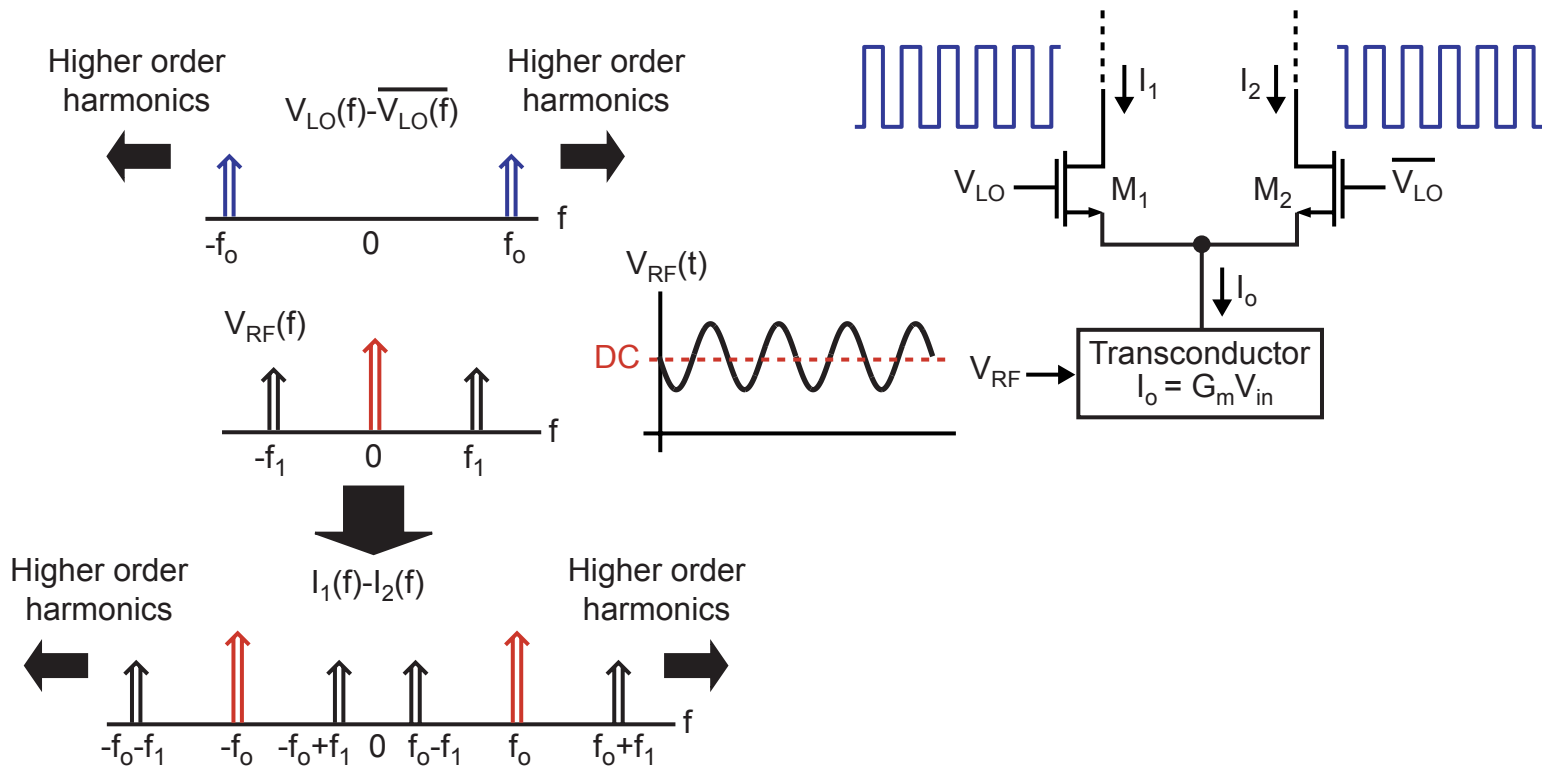
# LO Feedthrough in Single-Balanced Mixers



- **DC component of RF input causes very large LO feedthrough**
  - Can be removed by filtering, but can also be removed by achieving a zero DC value for RF input



# Double-Balanced Mixer

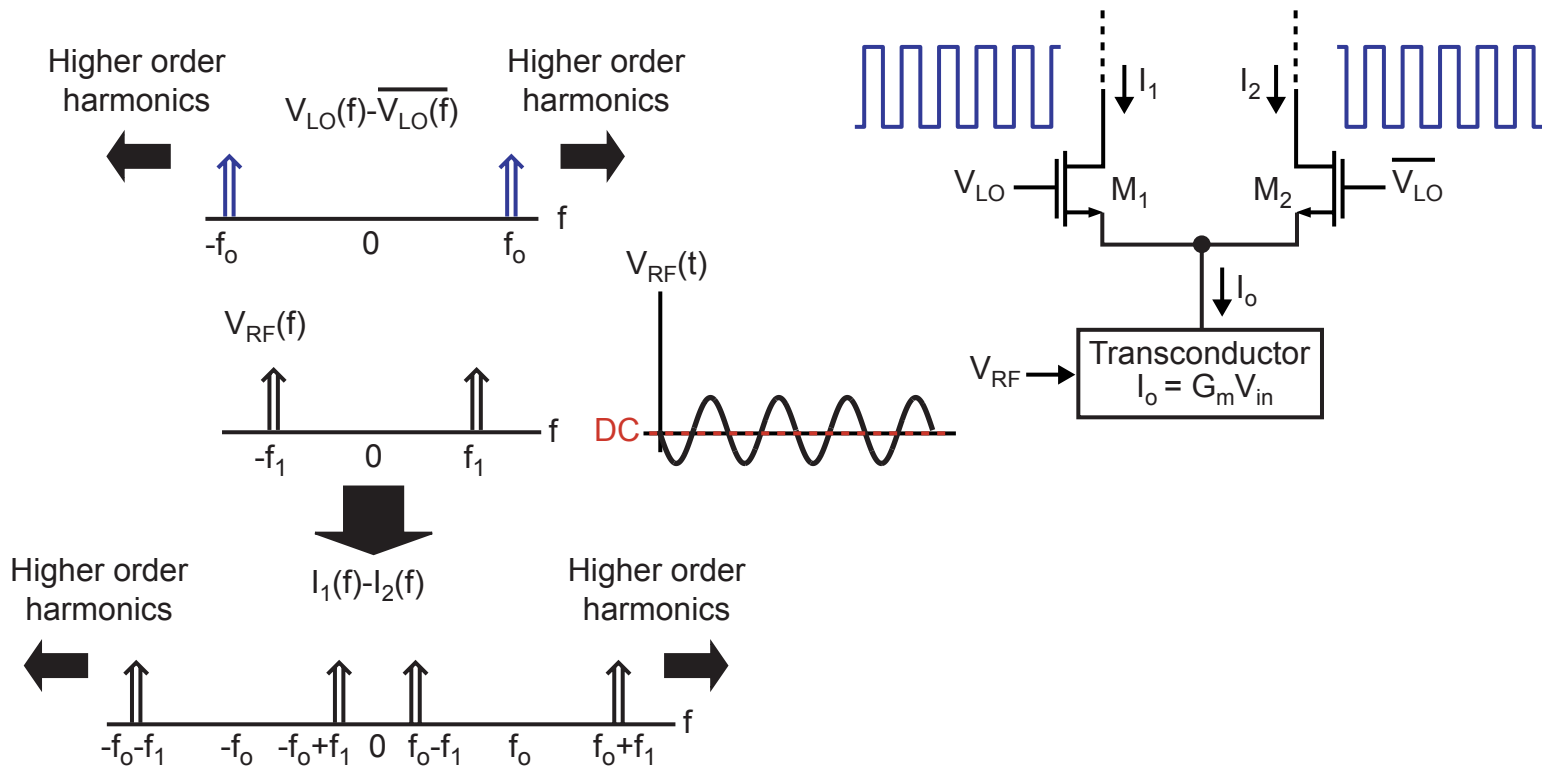


- DC values of LO and RF signals are zero (balanced)
- LO feedthrough dramatically reduced!
- But, practical transconductor needs bias current
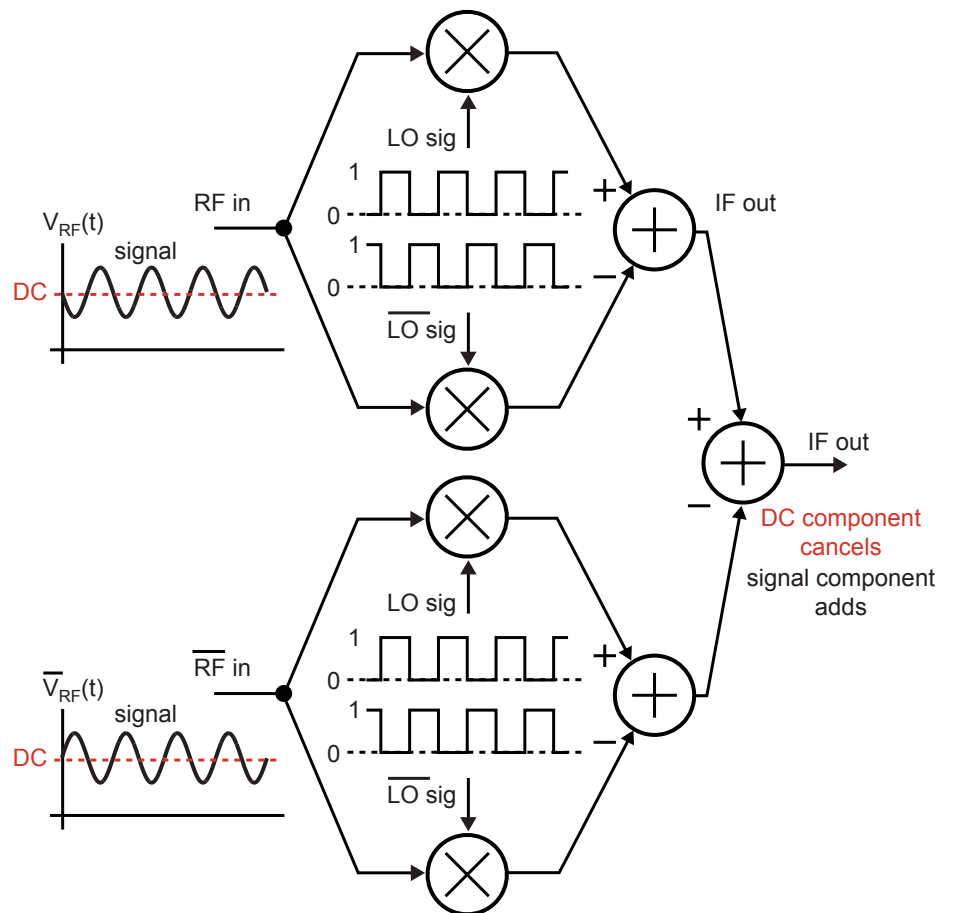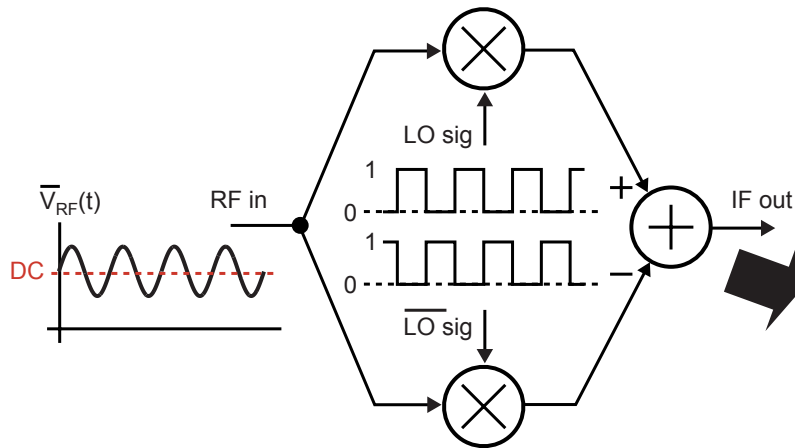
# Achieving a Balanced RF Signal with Biasing

- Use the same trick as with LO balancing



# Double-Balanced Mixer Implementation

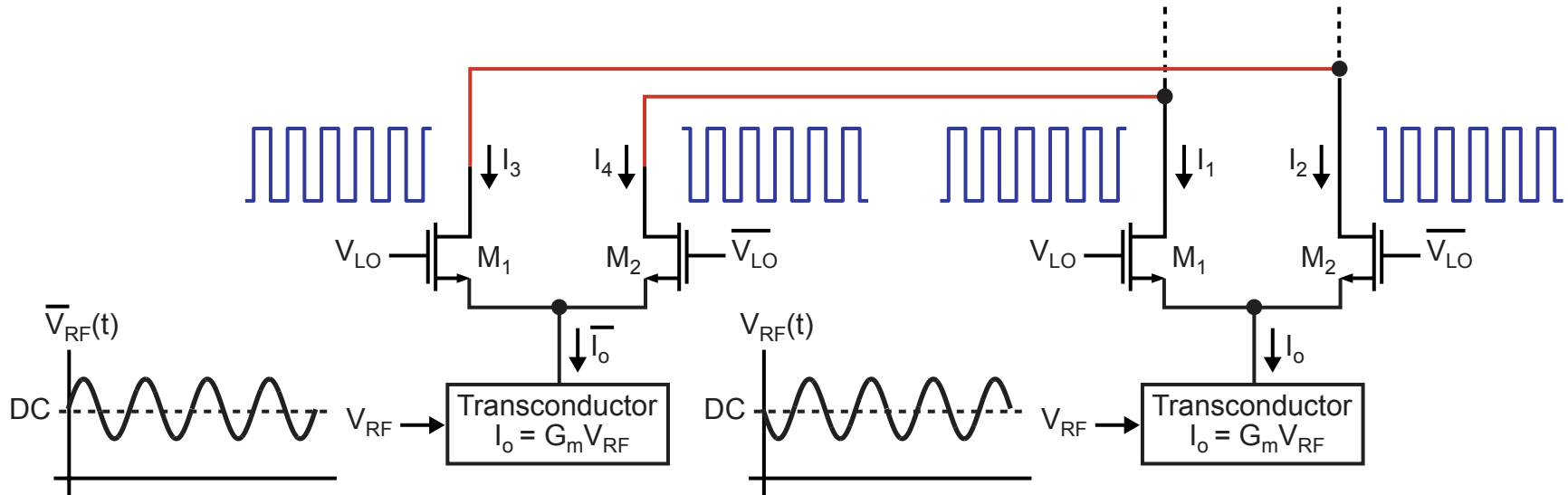


- Applies technique from previous slide
  - Subtraction at the output achieved by cross-coupling the output current of each stage






# A Highly Linear CMOS Mixer

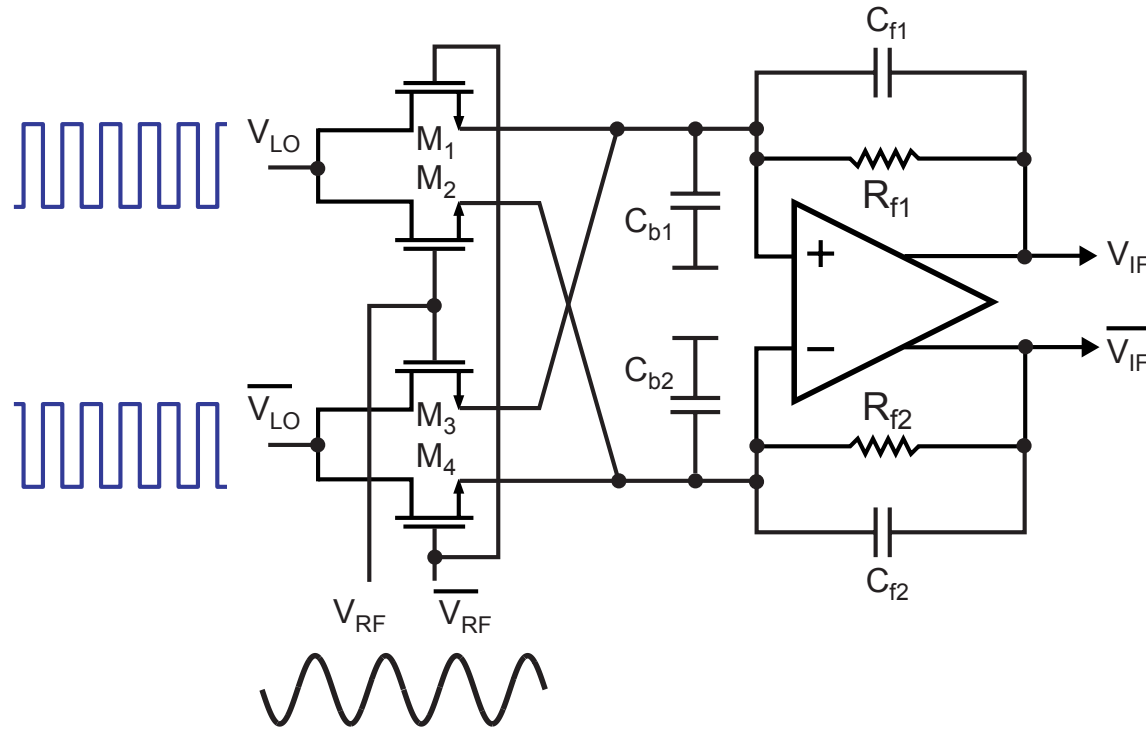


- Transistors are alternated between the off and triode regions by the LO signal
  - RF signal varies resistance of channel when in triode
  - Large bias required on RF inputs to achieve triode operation
- High linearity achieved, but very poor noise figure

# Passive Mixers

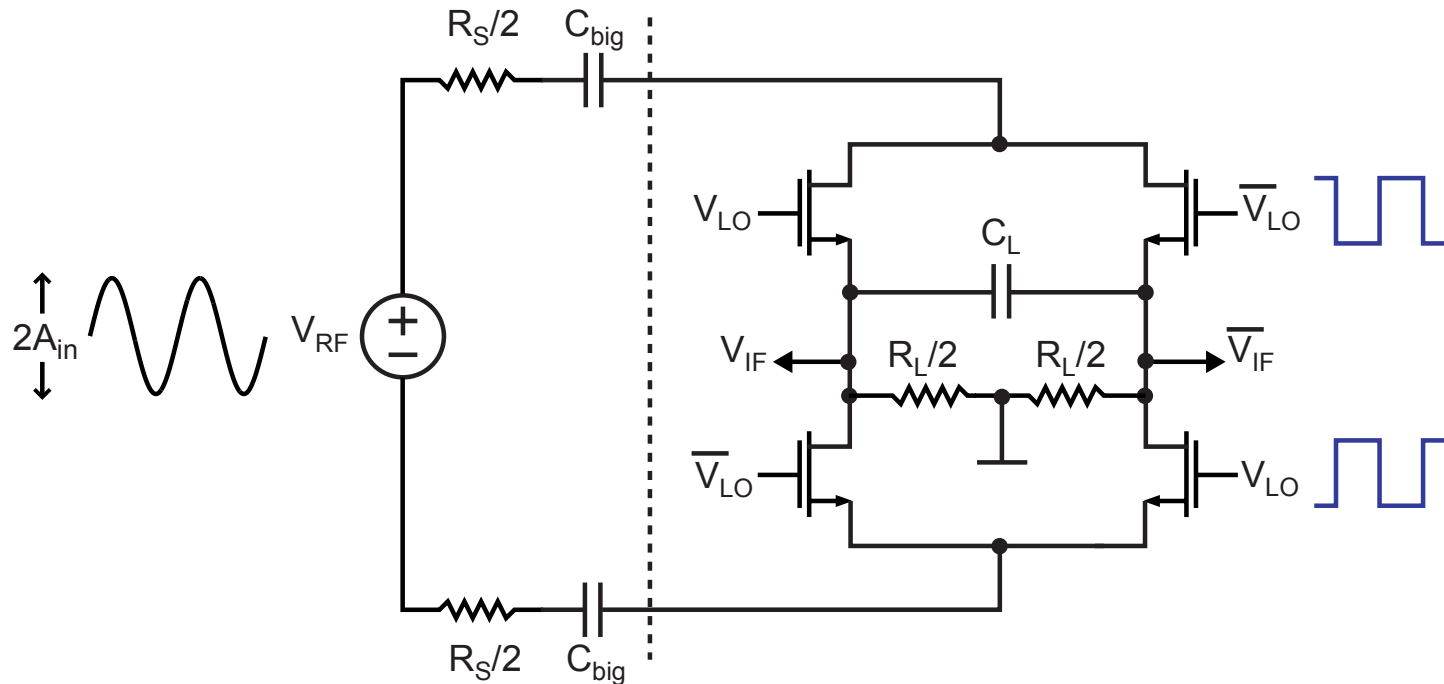


- We can avoid the transconductor and simply use switches to perform the mixing operation
  - No bias current required allows low power operation to be achieved
- You can learn more about it in Homework 4!

# Square-Law Mixer

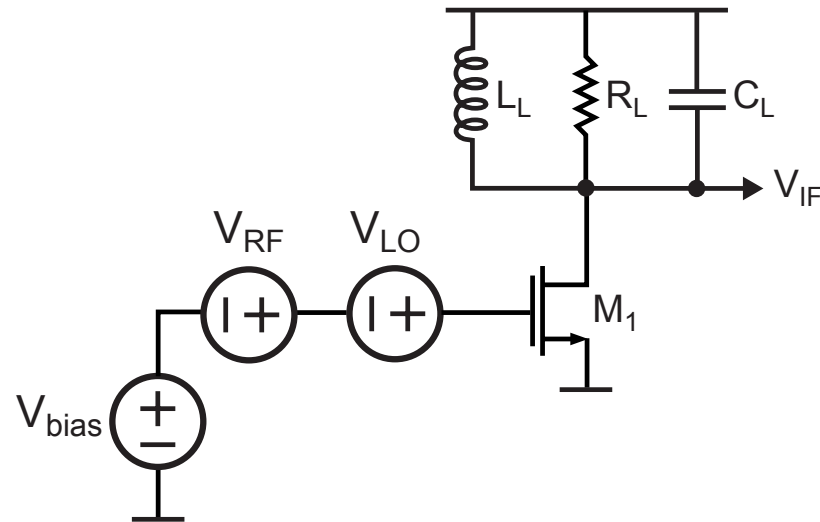

- Achieves mixing through nonlinearity of MOS device
  - Ideally square law, which leads to a multiplication term
$$(V_{RF} + V_{LO})^2 = V_{RF}^2 + 2V_{RF}V_{LO} + V_{LO}^2$$
  - Undesired components must be filtered out
- Need a long channel device to get square law behavior
- Issue – no isolation between LO and RF ports
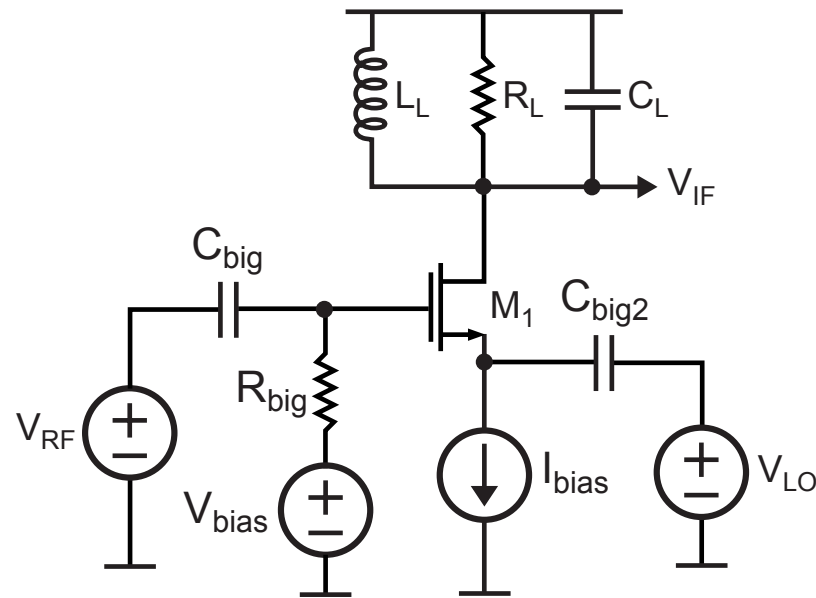
# Alternative Implementation of Square Law Mixer



- **Drives LO and RF inputs on separate parts of the transistor**
  - Allows some isolation between LO and RF signals
- **Issue - poorer performance compared to multiplication-based mixers**
  - Lots of undesired spectral components
  - Poorer isolation between LO and RF ports