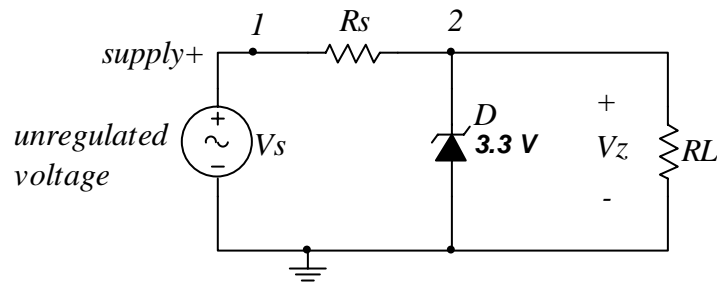


MASSACHUSETTS INSTITUTE OF TECHNOLOGY
6.071 Introduction to Electronics, Signals and Measurement
Spring 2006

Laboratory 17: Diodes: Signal conditioning: Voltage regulation

Voltage Regulator

The Zener diode with its well defined breakdown voltage may be used for building a very effective voltage regulator. In this exercise we will construct and test a voltage regulator circuit.



The supply is able to provide a maximum current of 1.5 A , and the Zener diode has an effective resistance of 30Ω .

Using $R_s \sim 500\Omega$ and $R_L \sim 10\text{ k}\Omega$ build the above circuit. From the class web site download the instrument called **ZenerRegulator**. This instrument controls the variable power supply of your ELVIS unit. Make the following connections to your protoboard.

Node 1: Connected to ACH1 (measures the unregulated voltage V_s)

Node 2: Connected to ACH2 (measures the regulated voltage V_z)

Run your instrument and observe the response of the circuit (regulated voltage V_z) as the unregulated voltage V_s is varied. Try adding noise to V_s and observe V_z .

Note the loading effect of this voltage regulator circuit. As V_s gets larger what is the max V_z across the load?


Given the maximum V_z and the diode's effective resistance calculate the maximum current through the diode I_z . What is the maximum current I_s ?

Voltage Level Protection.

The signal $V1$ generated by circuit 1 is transmitted to circuit 2 for further processing. However circuit 2 is very sensitive to voltage excursions above a certain level. In this example this voltage level is 6.6 Volts. The signal generated by circuit 1 is expected to be less than 6.6 Volts but it has been observed that certain transients that were not taken into consideration in the original design of circuit 1 may create voltage spikes greater than 6.6 Volts. These voltage spikes destroy circuit 2 and that is bad.


We would like to modify the circuit arrangement shown below so that the voltage seen by circuit 2 is always “clamped at 6.6 Volts.

Show your solution.

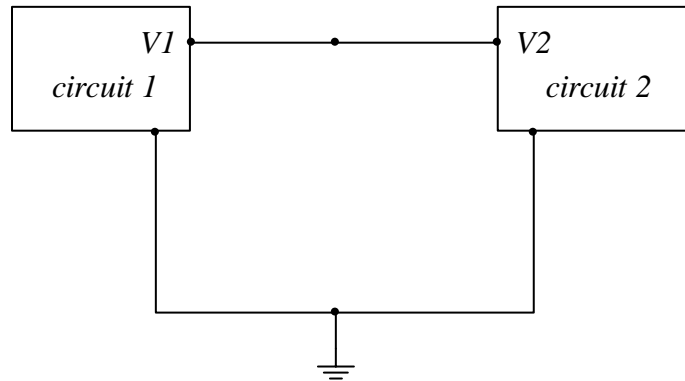


Peak Finder (and Keeper) Circuit

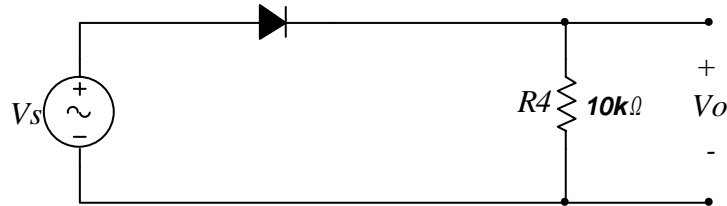The rectifier circuit studied in the previous lab consisted of a diode in series with a resistor as shown below.



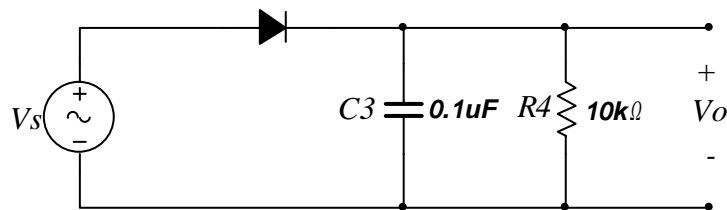Now by incorporating an energy storage element, the capacitor C_3 in the circuit below, the behavior of the circuit is modified in a very useful way.




For this exercise let's construct and test the circuit above. For V_s use the function generator and observe the input and output signals of your circuit with the oscilloscope. How are the amplitudes of V_s and V_o related?

What is the characteristic time τ_c of this circuit? (τ_c is the time it takes for a signal to fall to $1/e$ of its peak value or grow to $1 - 1/e$ of its peak value. In this case determine how the voltage V_o across C_3 decays as the capacitor dissipates power in R_4 when V_s is negative and the diode is off.)

Provide a signal V_s from your function generator and observe the output as a function of the frequency. In the space provided below, draw the superimposed signals V_s and V_o for the following frequencies: 5Hz, 50Hz, and 1kHz.

LED Voltage Level Indicator.

Consider the following circuit.

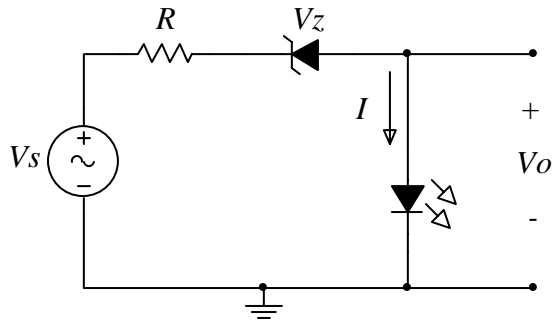

This circuit is constructed with a Zener diode an LED, a resistor and a voltage source.

Calculate the minimum voltage V_s that will turn the LED on. Assume that the forward voltage of the LED is V_g .

Build the circuit with a 3.3 Volt Zener diode.

Determine the value of R required to limit the current through the diodes to 10 mA.

For V_s start a triangular wave signal with a frequency 5 Hz varying from 0 to 5 Volts.

Observe the output voltage V_o .

Increase the frequency of V_s and determine the highest frequency that you can observe the blinking of the LED.