


MASSACHUSETTS INSTITUTE OF TECHNOLOGY
6.071 Introduction to Electronics, Signals and Measurement
 Spring 2006

Laboratory 18: Introduction to BJT

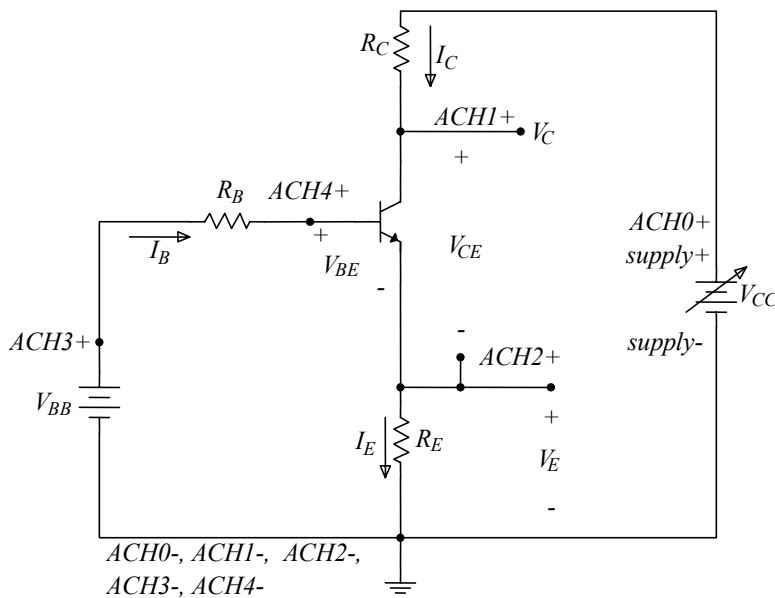
Exercise 1.


For this exercise, our first encounter with the BJT, we will explore its i-v characteristics with the aid of a prepared instrument. The instrument is called **BJT1.vi** and it is available for download from the Labs section.

Build the circuit shown below and make the connections as indicated on the schematic.




For the transistor we are using the 2N3904 npn BJT whose pinout is

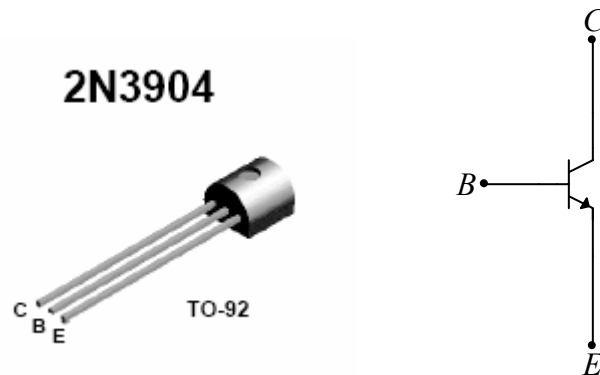

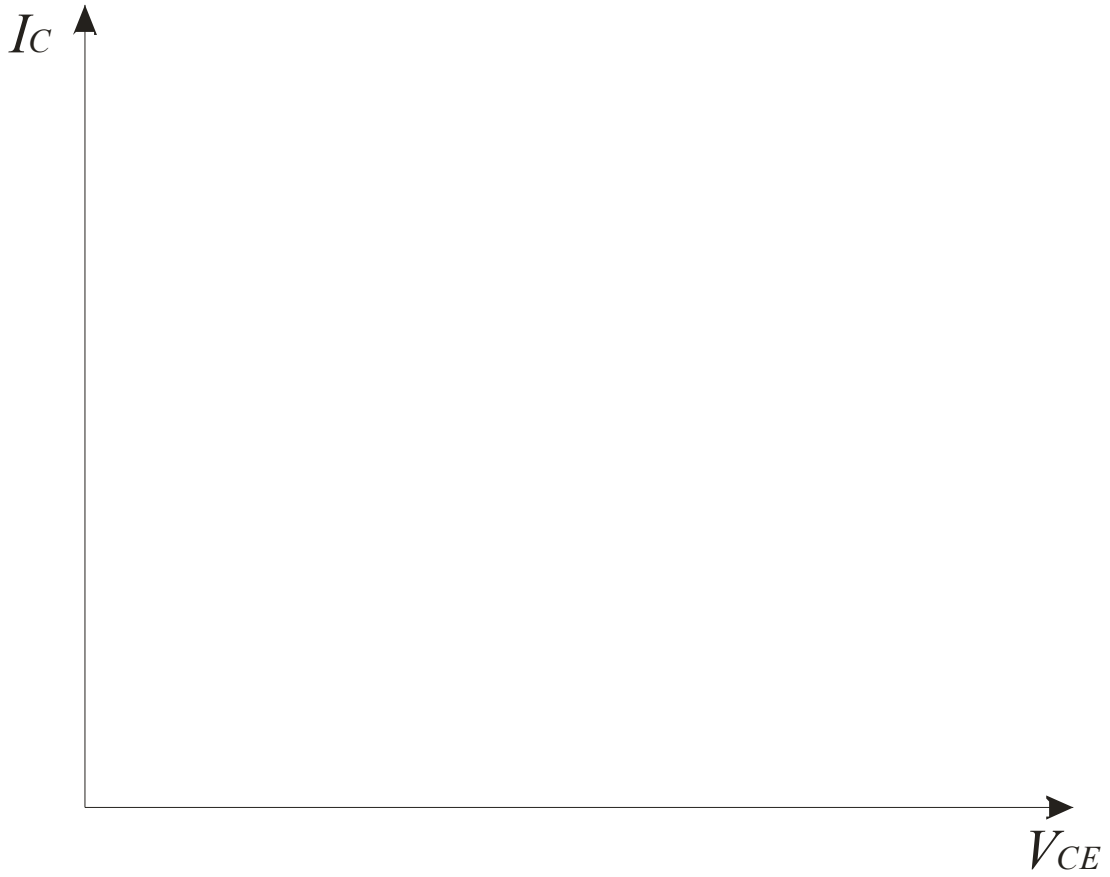

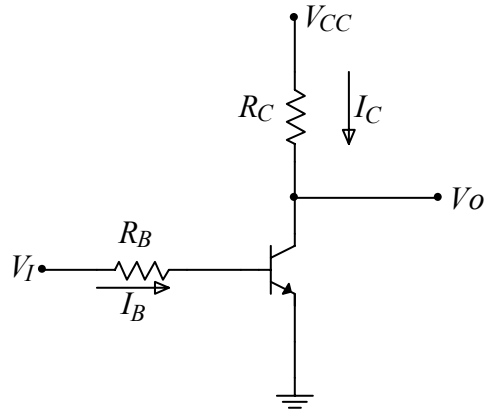Exercise 2.


Build the circuit shown below with $R_C=2k\Omega$ and $R_B=100k\Omega$.



For V_I use the variable power supply (supply+) and measure it and the voltage V_O with the oscilloscope.


For V_{CC} use +5 Volts.

Collect the data and plot them on the figure below. Indicate the relevant parameters and regions of operation.

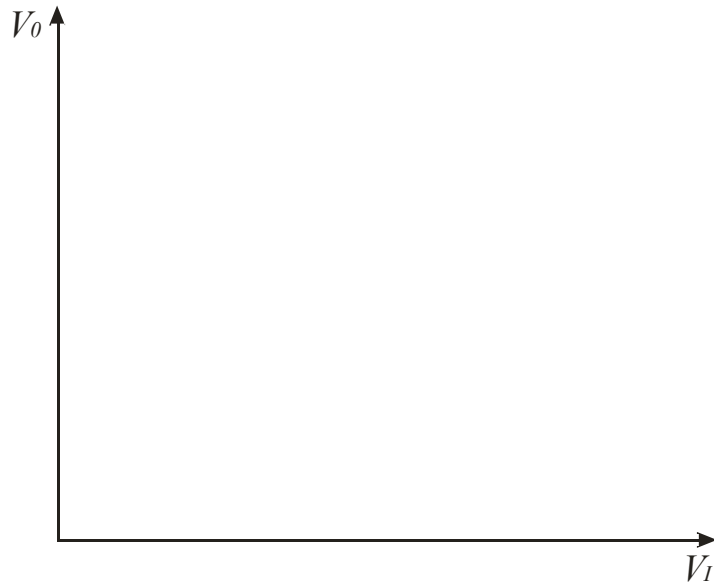

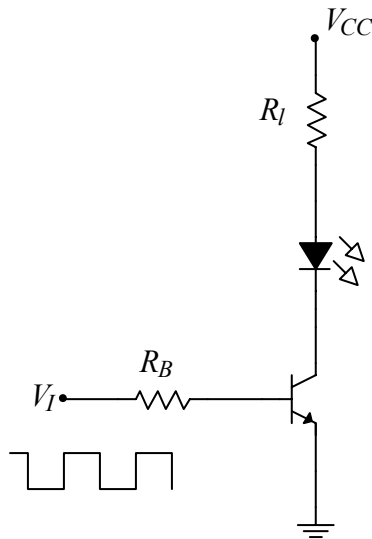Exercise 3. (For extra credit and only if you have time)

Now let's build the flashing circuit using a BJT. The circuit is shown below. For V_I use a square wave varying between 0 and 5 Volts and observe the output.



How does this compare with the diode flasher circuit that you tested previously?