
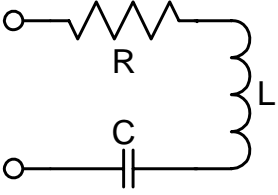


Impedance/Admittance Notation

$X_L = j\omega L$ $X_C = \frac{1}{j\omega C}$ $Z = R + j\omega L + \frac{1}{j\omega C}$ $Z = R + j\left[\omega L - \frac{1}{\omega C}\right]$ $Z = R + j[X_L - X_C]$ <hr style="border: 0.5px solid black;"/> <p><b>OHM's LAW:</b></p> $V = I R ; \quad V = I Z ;$ $V = I \left[ \frac{1}{Y} \right]; \quad V Y = I$	 $Z = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C}$ $Y = \frac{1}{Z}; \quad B_L = \frac{1}{X_L}; \quad B_C = \frac{1}{X_C}; \quad G = \frac{1}{R}$ $Y = G + \frac{1}{j\omega L} + j\omega C = G + j\left[\omega C - \frac{1}{\omega L}\right]$ $Y = G + j[B_C - B_L]$ 
--	---

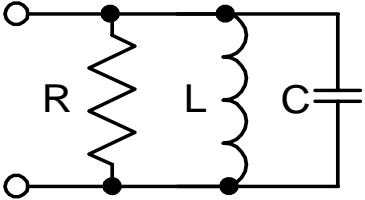Where does the  $\sqrt{2}$  or  $\frac{1}{\sqrt{2}}$  come from in  $-3\text{dB}$  point calculations?

