

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Mechanical Engineering

**2.004 Dynamics and Control II**  
Fall 2007

---

**Quiz 1**

Friday, October 5, 2007

PLEASE DO NOT TURN OVER UNTIL EXAM STARTS

TOTAL PAGES: 3

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
 Department of Mechanical Engineering  
**2.004 Dynamics and Control II**  
 Fall 2007


---

**Quiz 1**


Friday, October 5, 2007

**Duration: 50min** (11:05–11:55am)


A DC motor is connected to an op-amp circuit in cascade as shown in Figure 1. The op-amp circuit subsystem is shown in Figure 2; the input to the op-amp is a voltage source (battery)  $v_i(t)$ , the output is the voltage  $v_s(t)$ , and the transfer function of this subsystem is  $G_1(s)$ . The DC motor subsystem is shown in Figure 3; the input to the DC motor is the op-amp's output  $v_s(t)$ , the output is the angular velocity  $\omega(t)$  of a shaft connected to the motor, and the transfer function of this subsystem is  $G_2(s)$ . The DC motor subsystem is not loading the op-amp circuit subsystem. We will analyze the behavior of each subsystem independently, and that of the overall cascaded system.

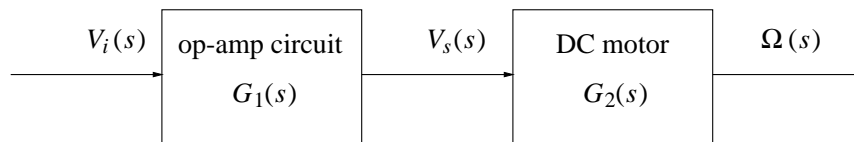

**Figure 1:** Cascade of an op-amp circuit subsystem and a DC motor subsystem.

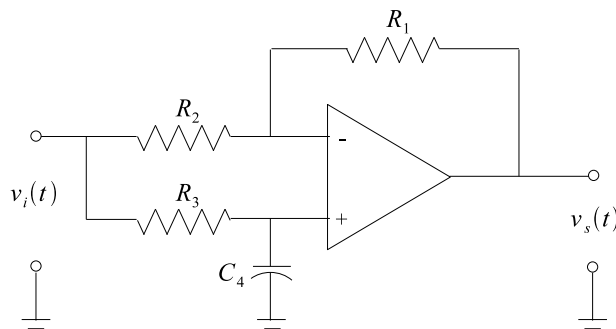

**Figure 2:** The op-amp circuit subsystem.

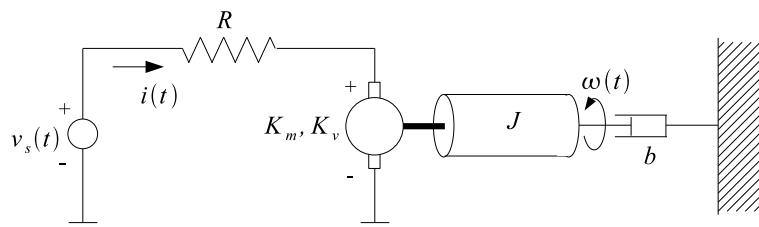


**Figure 3:** The DC motor subsystem.

Additional data for the op-amp circuit subsystem are: the resistors  $R_1 = 100\Omega$ ,  $R_2 = 100\Omega$  and  $R_3 = 100\text{ k}\Omega$ , and the capacitor  $C_4 = 1\mu F$ .

Additional data for the DC motor subsystem are: motor resistance  $R = 1\Omega$ ; the torque constant  $K_m = 1 \text{ N} \cdot \text{m} / \text{A}$  and back-emf constant  $K_v = 1 \text{ V} \cdot \text{sec} / \text{rad}$ ; the load shaft inertia  $J = 1 \text{ kg} \cdot \text{m}^2$  and viscous friction coefficient  $b = 1 \text{ N} \cdot \text{m} \cdot \text{sec} / \text{rad}$ . The motor's own inertia and inductance are negligible.

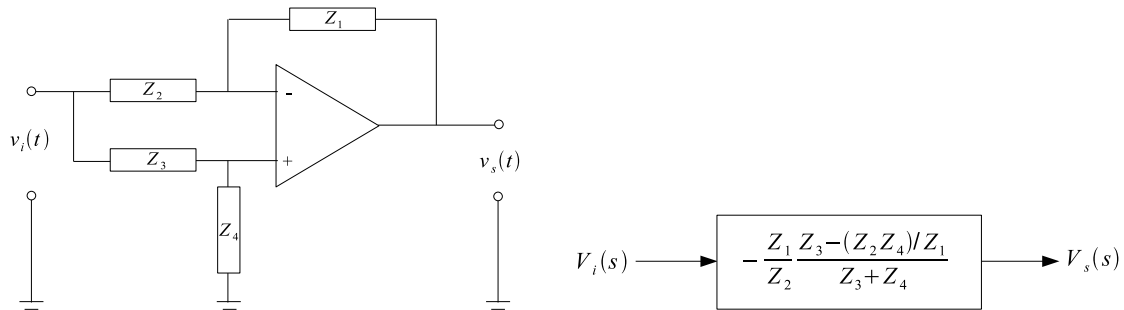1. (25%) Derive the transfer function  $G_1(s)$  of the op-amp circuit subsystem. Locate the poles and zeros of  $G_1(s)$  on the  $s$ -plane.
2. (25%) Derive the transfer function  $G_2(s)$  of the DC motor circuit subsystem. Locate the poles and zeros of  $G_2(s)$  on the  $s$ -plane.
3. (10%) Derive the overall system transfer function (*i.e.*, with  $V_i(s)$  as input and  $\Omega(s)$  as output.) Locate the poles and zeros of the overall system transfer function on the  $s$ -plane.
4. (25%) Derive the time-domain response  $\omega(t)$  when the input  $v_i(t)$  is a step function of amplitude 1V (*i.e.*, the unit-step response.)
5. (15%) Sketch the result that you obtained in question 4. What is the slope  $d\omega(t)/dt$  at  $t = 0+$  (*i.e.*, an infinitesimal amount of time after the switch is turned on?) Is that observation consistent with any features of the transfer function that you derived in question 3?

**Time-saving hint** You may use the following result to simplify your calculations: The voltage-in/voltage-out transfer function of an op-amp connected in feedback configuration with four impedances  $Z_1, Z_2, Z_3, Z_4$  is as shown below:




---

GOOD LUCK!

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Mechanical Engineering  
**2.004 Dynamics and Control II**  
Fall 2007

---

**Quiz 1 Solution**  
Friday, Oct. 5, '07

1. (25%) The transfer function  $G_1(s)$  of the op-amp subsystem.

*Answer:*

Let's denote  $V_a(s)$  as the voltage at the terminals of the op-amp. (Note the voltage is the same on both terminals.) From the voltage divider rule,  $V_a(s)$  can be written in the Laplace domain as

$$V_a(s) = \frac{1/C_4 s}{R_3 + 1/C_4 s} V_i(s).$$


Since no current may flow through the op-amp terminals, (*i.e.*, the input resistance is infinite) the current  $I_2$  flowing through  $R_2$  is the same as the current through  $R_1$ .

$$I_2 = \frac{V_i(s) - V_a(s)}{R_2} = \frac{V_a(s) - V_s(s)}{R_1}.$$

Substituting  $V_a$  in the above equations, solving for  $V_s$ , and substituting the numerical values, we obtain

$$G_1(s) = \frac{V_s(s)}{V_i(s)} = -\frac{R_1 s - R_2 / (R_1 R_3 C_4)}{R_2 s + 1 / (R_3 C_4)} = -\frac{s - 10}{s + 10}.$$

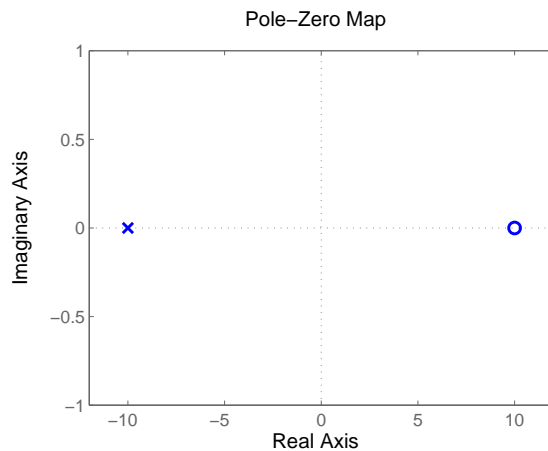Alternatively, we can get the same answer by direct substitution in the formula given as “time-saving hint.”



2. (25%) The transfer function  $G_2(s)$  of the DC motor subsystem.

*Answer:*

From KVL (in the Laplace domain),


$$V_s(s) - I(s)R - K_v\Omega(s) = 0.$$

From torque balance at the motor shaft,

$$K_m I(s) = (Js + b)\Omega(s).$$

Rearranging the above two equations, and substituting the numerical values, we obtain
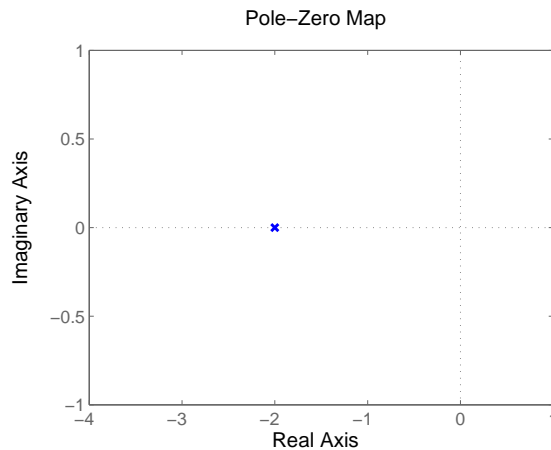
$$G_2(s) = \frac{\Omega(s)}{V_s(s)} = \frac{1}{s + 2}.$$




3. (10%) Overall system transfer function and location of poles and zeros.

*Answer:* Since the DC motor subsystem is not loading the op-amp circuit subsystem, the cascade transfer function is the product of the transfer functions of the two subsystems.

$$\begin{aligned} \frac{\Omega(s)}{V_i(s)} &= \frac{\Omega(s)}{V_s(s)} \times \frac{V_s(s)}{V_i(s)} = G_2(s) \cdot G_1(s) \\ &= -\frac{s - 10}{(s + 10)(s + 2)} \end{aligned}$$

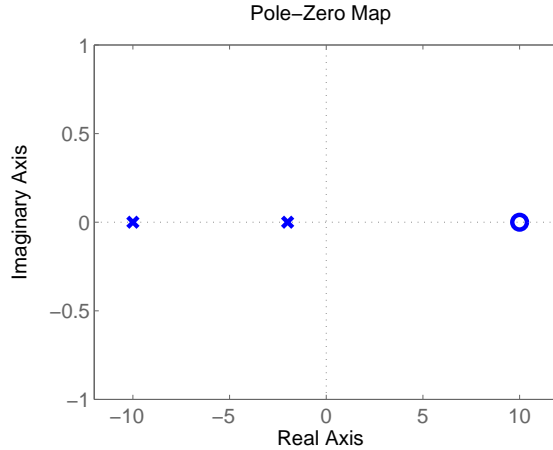Poles:  $p_1 = -10$  and  $p_2 = -2$ . Zero:  $z_1 = +10$ . At this point we may already observe that the two poles are on the left-hand half-plane, so the system is stable; but the zero is on the right-hand half-plane, so the system is non-minimum phase (we'll pick up again on that point in question 5.)



4. (25%) Time domain-step response.

*Answer:* We can see from the transfer function that this is a second order system with two real & negative poles; therefore, we recognize an overdamped system. To obtain the step response, we multiply the transfer function by  $1/s$ , *i.e.* the Laplace transform of the unit step function, and expand in partial fractions.

$$-\frac{s - 10}{s(s + 2)(s + 10)} = \frac{A}{s} + \frac{B}{s + 2} + \frac{C}{s + 10}.$$

The partial fraction expansion works out as follows:

$$\begin{aligned} A &= -\left. \frac{s - 10}{(s + 2)(s + 10)} \right|_{s=0} = \frac{1}{2}; \\ B &= -\left. \frac{s - 10}{s(s + 10)} \right|_{s=-2} = -\frac{3}{4}; \\ C &= -\left. \frac{s - 10}{s(s + 2)} \right|_{s=-10} = +\frac{1}{4}. \end{aligned}$$

Therefore, the Laplace transform of the step response is:

$$\frac{1/2}{s} - \frac{3/4}{s + 2} + \frac{1/4}{s + 10}.$$

From this, we obtain immediately the step response in the time domain

$$f(t) = \left( \frac{1}{2} - \frac{3}{4}e^{-2t} + \frac{1}{4}e^{-10t} \right) u(t).$$

5. (15%) Sketch the time response.

*Answer:* Looking at the limit  $t \rightarrow \infty$  in the time-domain step response (or, equivalently, using the final value theorem on the Laplace transform of the step

response) we find that the steady-state value of the step response is  $1/2$ . Since this is an overdamped system, and there is no clear dominant pole, the response will approach the steady-state value asymptotically but we cannot easily specify by hand the time constant.

We can, however, say more about the behavior of the step response at small times ( $t = 0+$ .) Since the system is non-minimum phase (*i.e.*, it has a zero on the right-hand half-plane), we should be worried that its step response might initially head in the opposite direction (negative) than the steady-state value (positive.) We verify this by computing the slope (derivative  $d\omega(t)/dt$ ) of the step response at  $t = 0+$ , as asked by the problem statement. Using the initial value theorem,

$$\mathcal{L} \left[ \frac{d\omega}{dt} \right] = sF(s).$$

$$\left. \frac{d\omega}{dt} \right|_{t=0+} = \lim_{s \rightarrow \infty} s(sF(s)) = \lim_{s \rightarrow \infty} -s \frac{s(s-10)}{s(s+2)(s+10)} = +1.$$

(Note: alternatively, we can get the same answer by direct differentiation of the time-domain step response that we derived in question 4.) Indeed, the system exhibits an “undershoot,” *i.e.* the motor starts rotating in the opposite direction (negative) than its steady-state value (positive.)

We have plotted below the exact response of the system using MATLAB . In your answer sheet, you should have drawn something that looks *approximately* like this, indicating the undershoot and the steady-state value.

