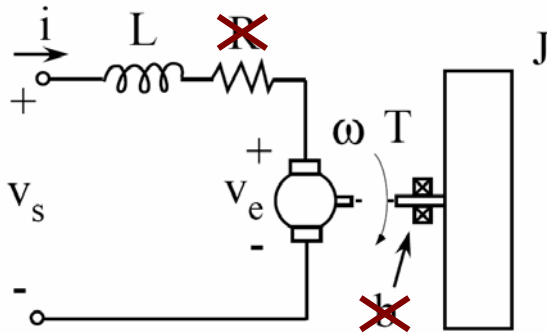


Undamped DC motor system: complete response



Electro-mechanical equations of motion (time domain)

$$L \frac{di}{dt} + \cancel{R} + K_v \omega = v_s$$

$$J \frac{d\omega}{dt} + \cancel{B} = K_m i$$

Step-function source


$$v_s(t) = V_0 u(t).$$

$$L = 0.1\text{H}, J = 2\text{kg} \cdot \text{m}^2,$$


$$K_v = 6\text{V} \cdot \text{sec}, K_m = 6\text{N} \cdot \text{m/A},$$

$$V_0 = 30\text{V}.$$

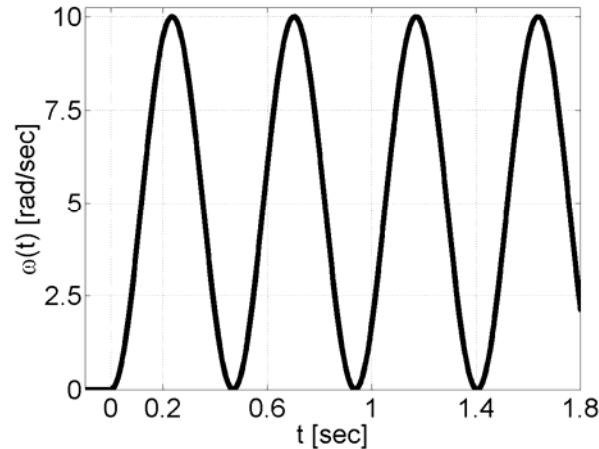
$$\omega(t) = \frac{V_0}{K_v} (1 - \cos(\omega_n t)).$$



$$v_e(t) = K_v \omega(t).$$

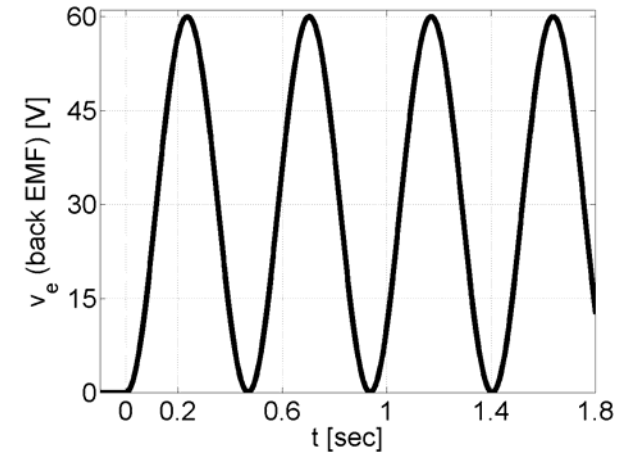
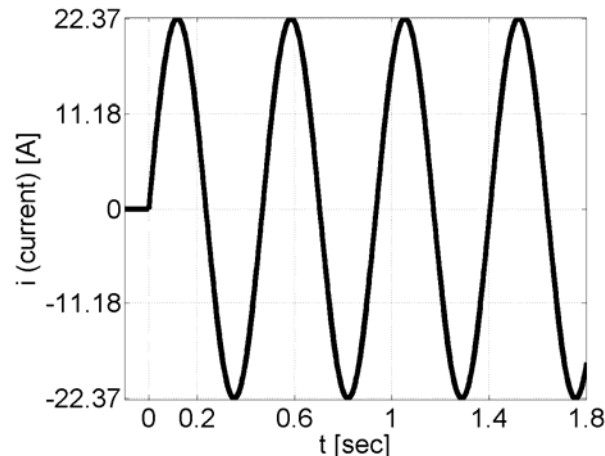
$$i(t) = \frac{J}{K_m} \frac{d\omega(t)}{dt}.$$



$$v_L(t) = L \frac{di(t)}{dt} = v_s(t) - v_e(t).$$

